



**MANIPAL UNIVERSITY
JAIPUR**

(University under Section 2(f) of the UGC Act)



B.TECH FIRST YEAR

ACADEMIC YEAR: 2023-2024



COURSE NAME: EES

COURSE CODE : EE 1002

LECTURE SERIES NO :

CREDITS : 4

MODE OF DELIVERY : (POWER POINT PRESENTATION)

FACULTY

EMAIL-ID

PROPOSED DATE OF DELIVERY:



**MANIPAL UNIVERSITY
JAIPUR**

VISION

Global Leadership in Higher Education and Human Development

MISSION

- Be the most preferred University for innovative and interdisciplinary learning
- Foster academic, research and professional excellence in all domains
- Transform young minds into competent professionals with good human values


VALUES

Integrity, Transparency, Quality,
Team Work, Execution with Passion, Humane Touch

OPERATIONAL AMPLIFIER (OP- AMP)

Reference Book:

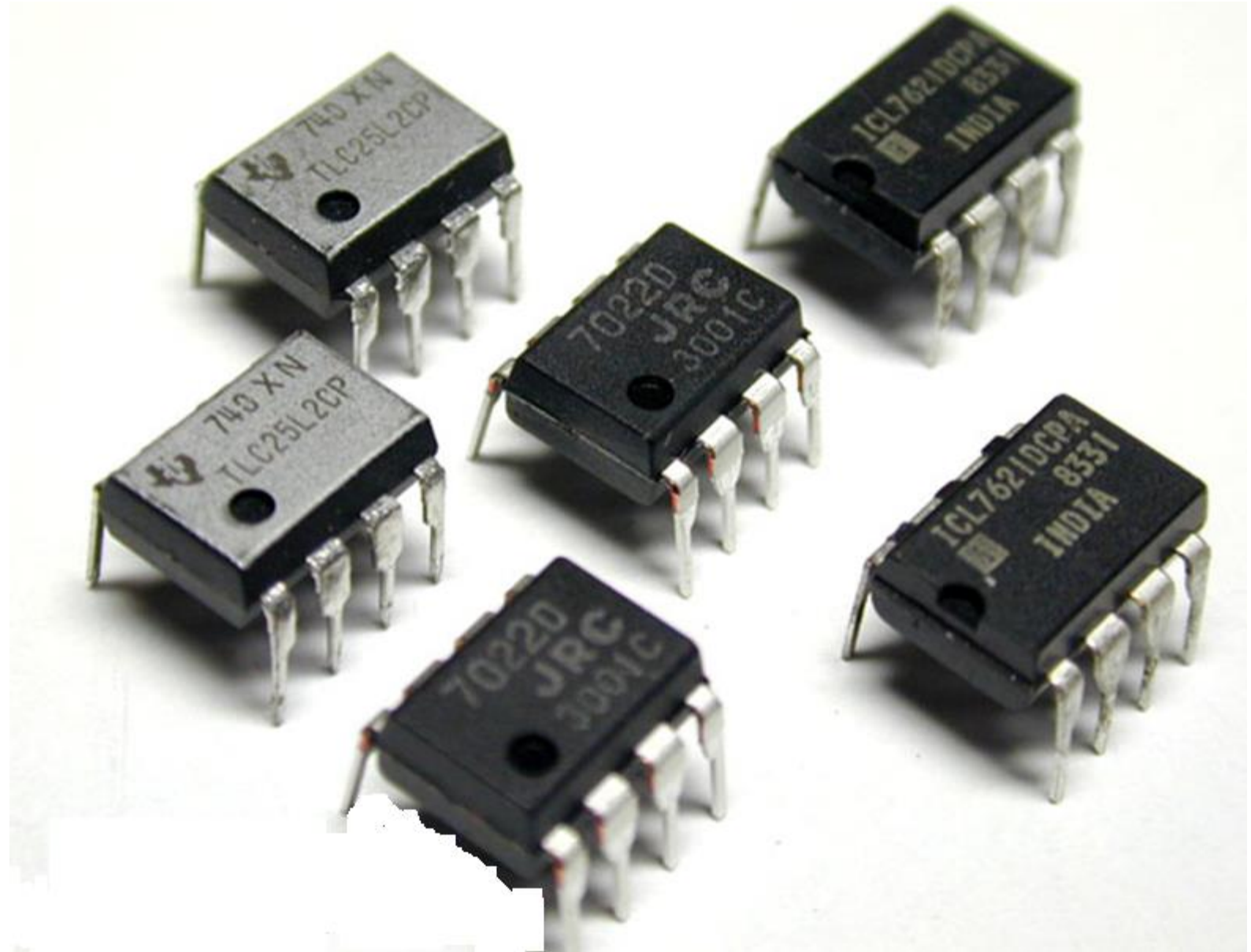- 1. OPAMPS and Linear Integrated Circuits
by Ramakanth Gayakwad



CONTENTS

- Introduction
- OPAMP Symbol
- Internal block diagram
- Open-loop configuration
- Common mode rejection ratio
- OPAMP equivalent circuit
- OPAMP characteristics


INTRODUCTION

- Operational Amplifier (OPAMP) is a direct coupled high-gain amplifier fabricated on Integrated Circuit (IC)
- Op-amps are linear devices that are ideal for DC and AC amplification and are used often in signal conditioning, filtering .
- Earlier, op-amp were used primarily to perform mathematical operation such as summation, subtraction, differentiation and integration etc. so named as op-amp.
- Typical application of op-amp includes –
 1. Audio amplifier-voltage amplitude change
 2. Signal generators- oscillators,
 3. Signal filter circuits
 4. Instrumentation circuits---Biomedical Instrumentation

INTRODUCTION

- Advantages of OP-AMP over transistor amplifier
 - Less power consumption
 - Costs less
 - More compact, fabricated in a single chip.
 - More reliable
 - Higher gain can be obtained
 - Easy design

OPAMP TERMINALS

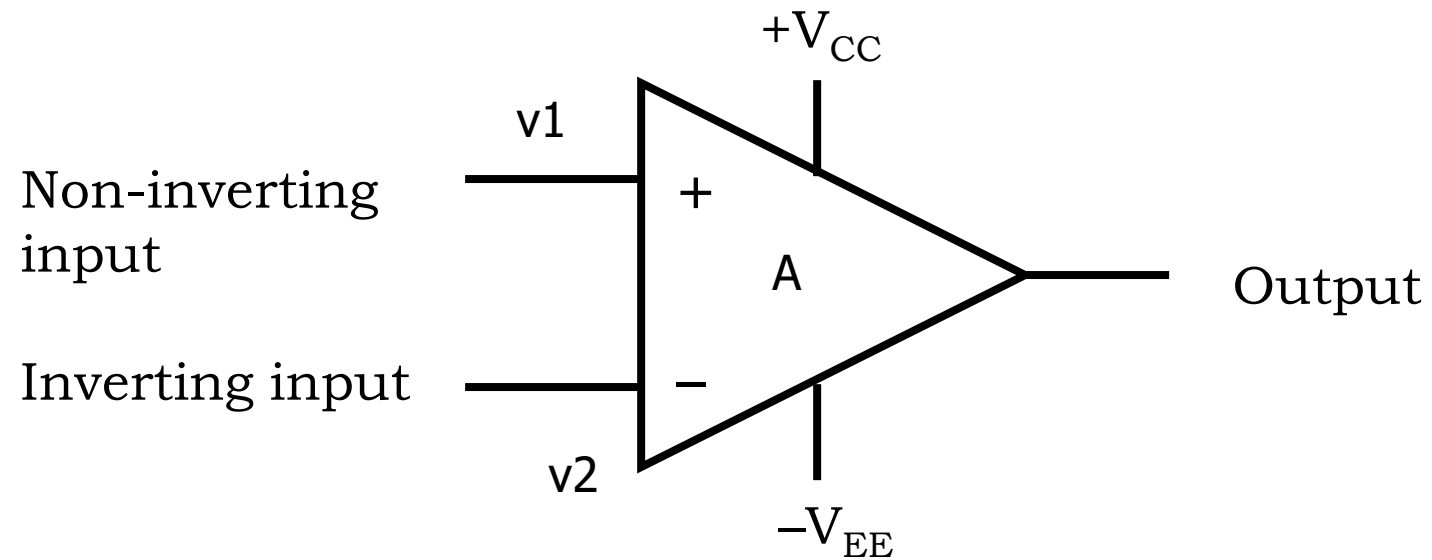


Here, A = Large signal voltage gain

OP-AMP TERMINALS


- If input is applied to non-inverting input terminal, then output will be in-phase with input
- If input is applied to inverting input terminal, then output will be 180 degrees out of phase with input
- If inputs are applied to both terminals, then output will be proportional to difference between the two inputs

OPAMP TERMINALS

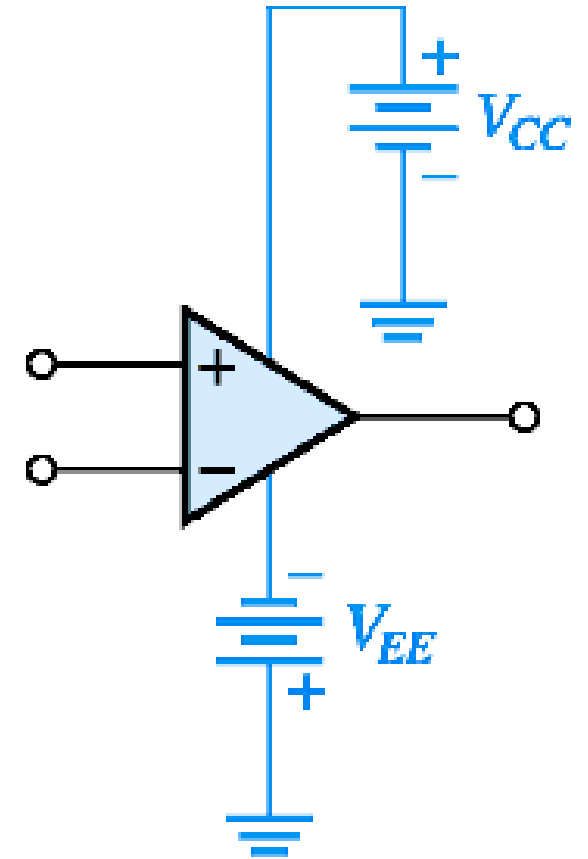- Two DC power supplies (dual) are required
- Magnitudes of both may be same
- The other terminal of both power supplies are connected to common ground
- All input and output voltages are measured with reference to the common ground




OPAMP TERMINALS

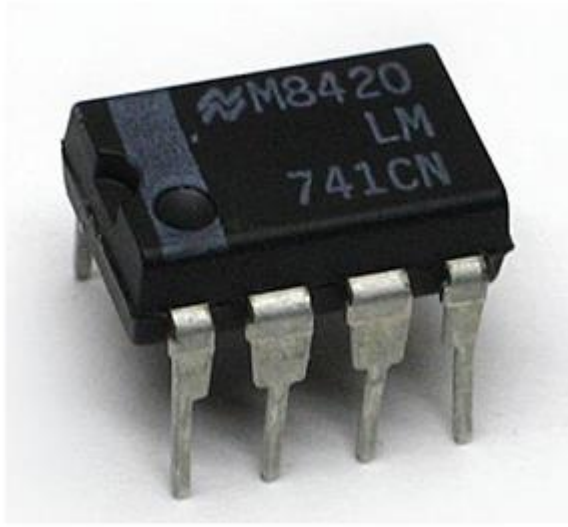

Integrated Circuit

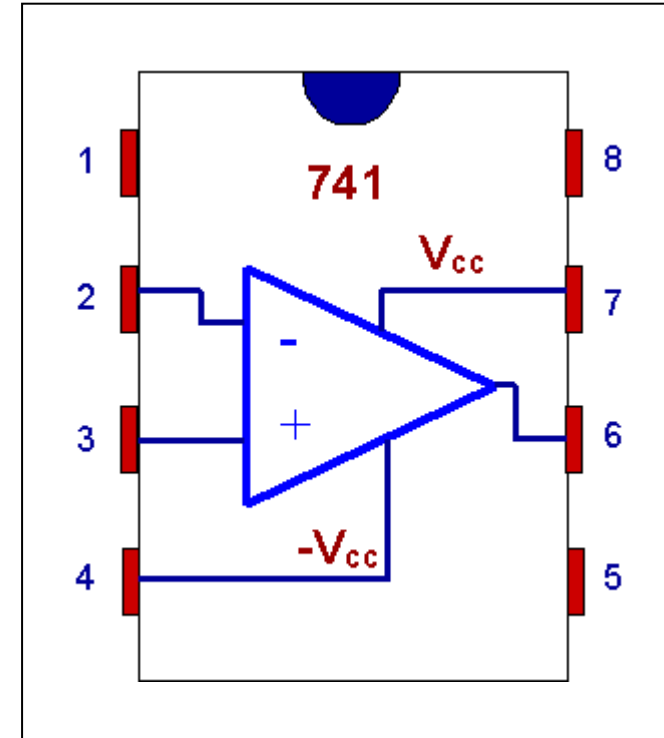
- Pin 1 & 5 Offset null
- Pin 2 & 3 input
- Pin 4 & 7 VCC



Pin Diagram

- | | |
|-------|---------------|
| Pin 6 | Output |
| Pin 8 | Not connected |

INTERNAL BLOCK DIAGRAM

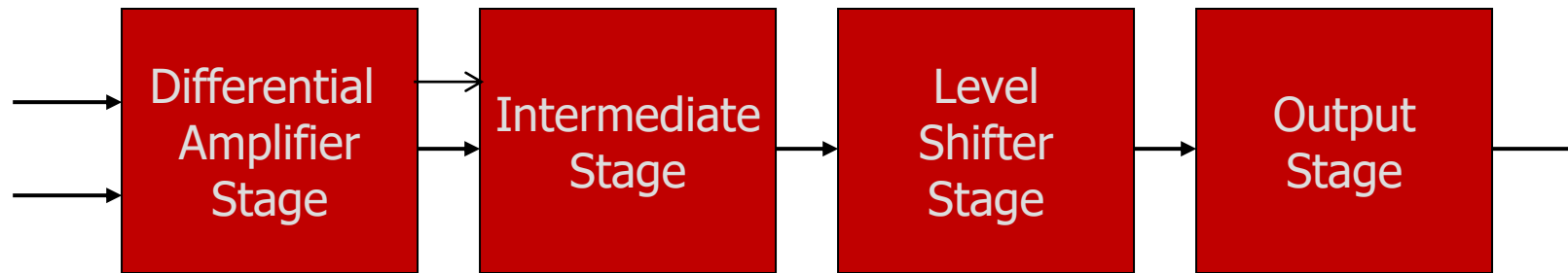

Dual input,
Balanced output
Differential amplifier

Dual input
unbalanced output
Differential amplifier

Such as
emitter follower
Using constant
current source


Complementary
symmetry
push-pull amplifier

INTERNAL BLOCK DIAGRAM

Four stages can be identified –

- Input stage or differential amplifier stage can amplify difference between two input signals; Input resistance is very high; Draws zero current from the input sources
- Intermediate stage (or stages) use direct coupling; provide very high gain
- Level shifter stage shifts the dc level of output voltage to zero (can be adjusted manually using two additional terminals)
- Output stage is a power amplifier stage; has very small output resistance; so output voltage is the same, no matter what is the value of load resistance connected to the output terminal

OPEN-LOOP CONFIGURATION

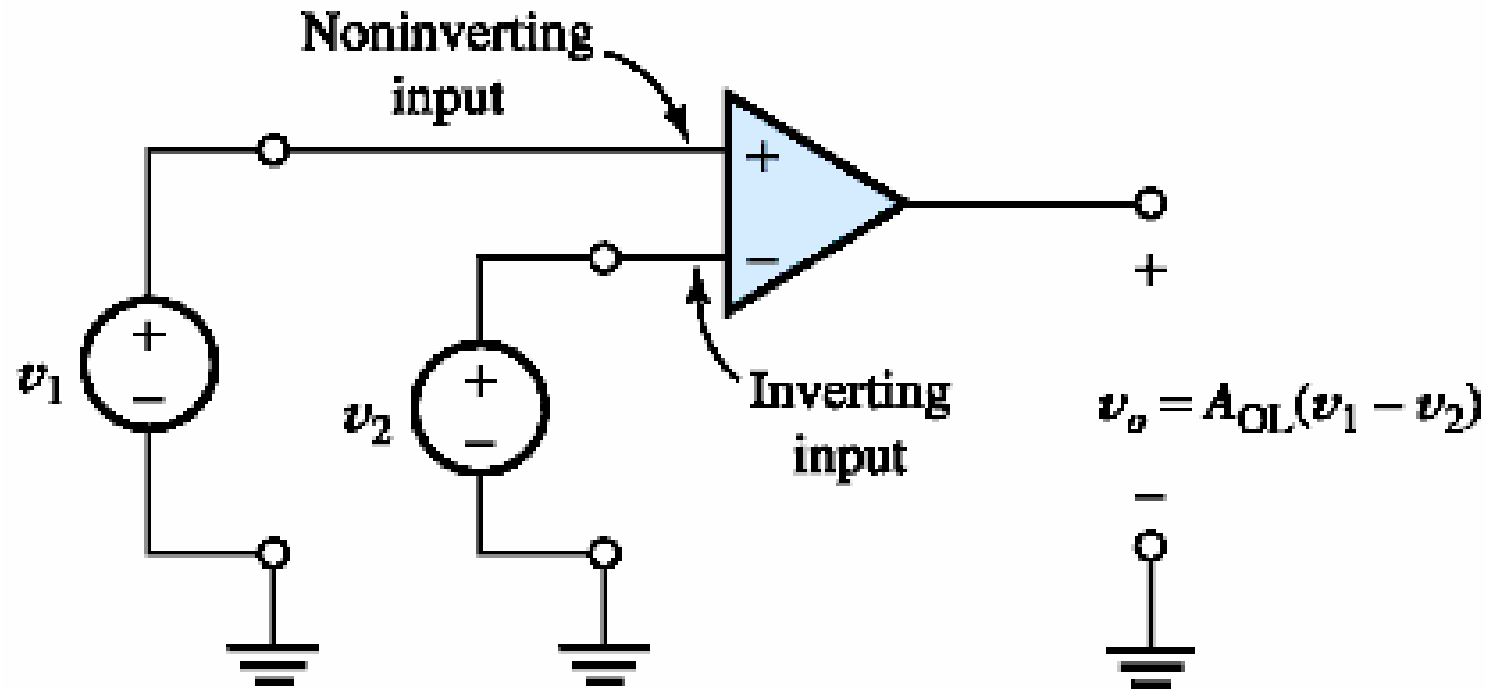

If $v_1 = 0$, then $v_o = -A_{OL}v_2$ Inverting amplifier

If $v_2 = 0$, then $v_o = A_{OL}v_1$ Non-inverting amp

OPEN-LOOP CONFIGURATION

- A_{OL} is the open-loop voltage gain of OPAMP
Its value is very high
Typical value is 0.5 million
- So, even if input is in micro volts, output will be in volts
- But output voltage cannot cross the value of power supply V_{CC}
- So, if input is in milli volts, output reaches saturation value $V_{sat} = V_{CC}$ (or V_{EE})

OPEN-LOOP CONFIGURATION

- If $v_1 = v_2$, then ideally output should be zero
- But in practical Op-Amp, output is

$$v_o = A_{cm} \left(\frac{v_1 + v_2}{2} \right)$$

Where, A_{CM} is the common-mode gain of Op-Amp

- So, final gain equation is:

$$v_o = A_d (v_1 - v_2) + A_{cm} \left(\frac{v_1 + v_2}{2} \right)$$

$$v_o = A_d v_{id} + A_{cm} v_{icm}$$

OPEN-LOOP CONFIGURATION

- Common-mode rejection ratio
 - It is a measure of the ability of Op-Amp to reject the signals common to both input terminals (noise)
 - Defined as

$$CMRR = \frac{A_d}{A_{cm}}$$

$$(CMRR)_{dB} = 20 \log_{10} \left(\frac{A_d}{A_{cm}} \right)$$

PROBLEMS

- An OPAMP has differential voltage gain of 100,000 and CMRR of 60 dB. If non inverting input voltage is $150\text{ }\mu\text{V}$ and inverting input voltage is $140\text{ }\mu\text{V}$, calculate the output voltage of OPAMP


Ans: 1.01 V

- For an OPAMP, when v_1 is 0.5 mV and v_2 is -0.5 mV , output voltage is 8 V. For the same OPAMP, when $v_1 = v_2 = 1\text{ mV}$, output voltage is 12 mV. Calculate the CMRR of the OPAMP

Ans: 56.48 dB

OPAMP equivalent circuit

Practical OPAMP

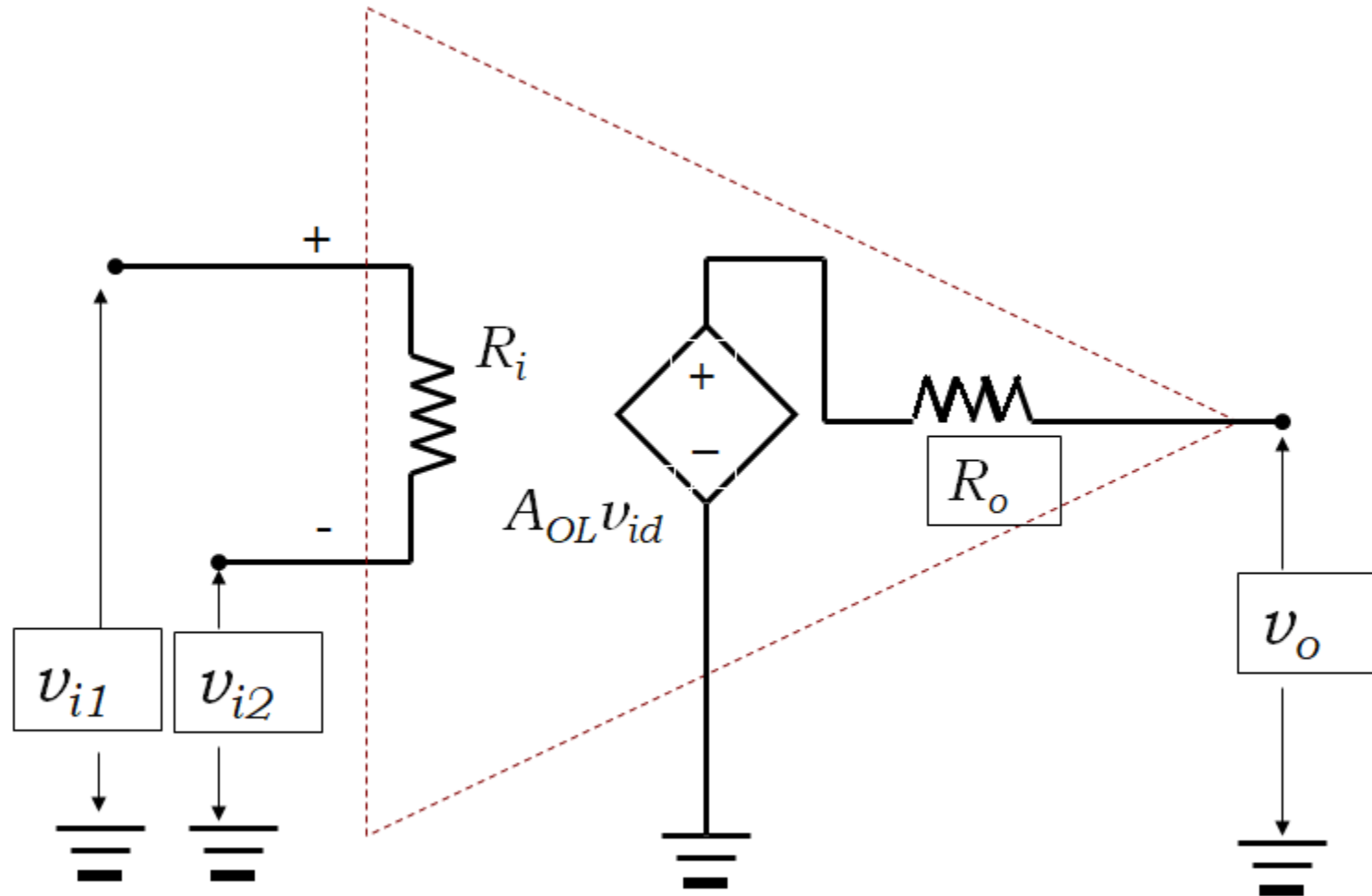

OPAMP CHARACTERISTICS

- Differential mode gain A_d
 - It is the factor by which the difference between the two input signals is amplified by the OPAMP
- Common mode gain A_{cm}
 - It is the factor by which the common mode input voltage is amplified by the OPAMP
- Common mode rejection ratio $CMRR$
 - Is the ratio of A_d to A_{cm} expressed in decibels

OPAMP CHARACTERISTICS

- Input resistance R_i
 - It is the equivalent resistance measured between the two input terminals of OPAMP
- Output resistance R_o
 - It is equivalent resistance measured between output terminal and ground
- Bandwidth
 - It is the range of frequency over which the gain of OPAMP is almost constant

OPAMP CHARACTERISTICS

- Output offset voltage V_{oo}
 - It is the output voltage when both input voltages are zero
 - Denoted as V_{oo}
- Input offset voltage V_{io}
 - It is the differential input voltage that must be applied at the input terminals in order to make output voltage equal to zero
 - $V_{io} = |v_{dc1} - v_{dc2}|$ for $v_o = 0$

OPAMP CHARACTERISTICS

- Input offset current I_{io}
 - It is the difference between the currents in the input terminals when both input voltages are zero
 - $I_{io} = | I_1 - I_2 |$ when $v_1 = v_2 = 0$
- Input bias current I_{ib}
 - It is the average of the currents in the input terminals when both input voltages are zero
 - $I_{ib} = (I_1 + I_2) / 2$ when $v_1 = v_2 = 0$

OPAMP CHARACTERISTICS

- Slew rate SR
 - It is the maximum rate of change of output voltage with respect to time
 - Slew rate has to be very high if OPAMP has to operate efficiently at high frequencies
- Supply voltage rejection ratio $SVRR$
 - It is the maximum rate at which input offset voltage of OPAMP changes with change in supply voltage

OPAMP CHARACTERISTICS

■ Practical characteristics of 741C OPAMP

- Differential mode gain is 200,000
- CMRR is 90 dB
- Input resistance is 2 M Ω
- Output resistance is 75 Ω
- Unity-gain Bandwidth is 1 MHz
- Slew rate is 0.5 V / μ s
- Output offset voltage is 1 mV
- Input offset current is 20 nA
- Input bias current is 80 nA

■ Ideal OPAMP

- Infinite differential mode gain
- Zero common mode gain
- Infinite CMRR
- Infinite input resistance
- Zero output resistance
- Infinite bandwidth
- Infinite slew rate
- Zero input offset voltage
- Zero input offset current
- Zero output offset voltage