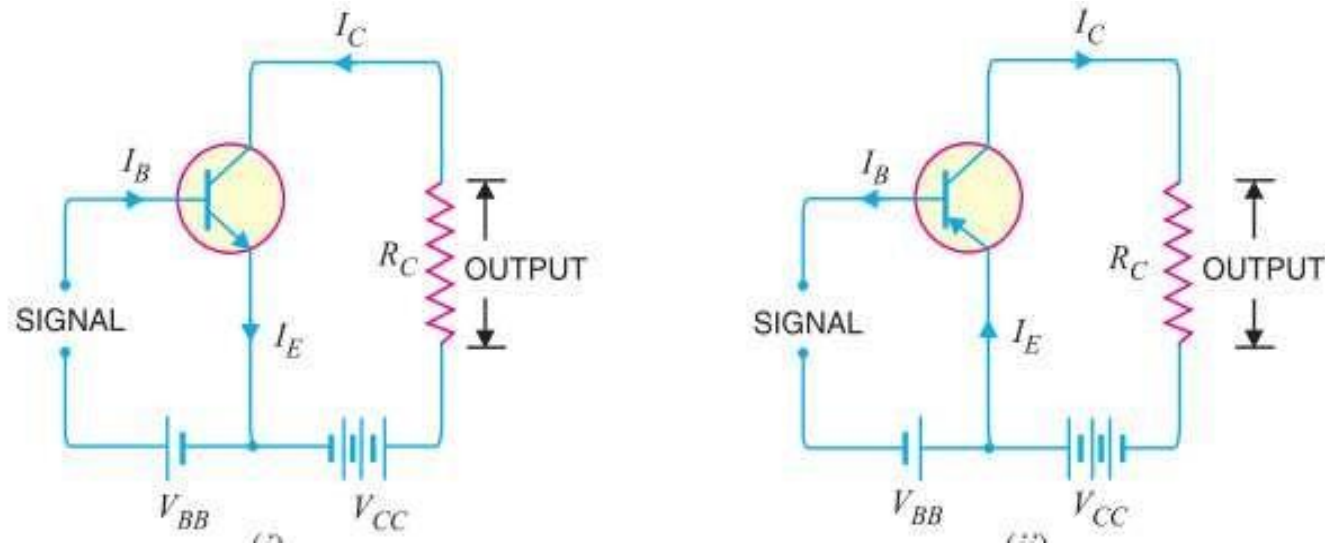


COMMON EMITTER CONNECTION

- The common-emitter terminology is derived from the fact that the emitter is common to both the input and output sides of the configuration.



- First Figure shows common emitter npn configuration and second figure shows common emitter pnp configuration.

COMMON EMITTER CONNECTION

- Base Current amplification factor (β) :
- In common emitter connection input current is base current and output current is collector current.
- The ratio of change in collector current to the change in base current is known as base current amplification factor, β .

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

- Normally only 5% of emitter current flows to base, so amplification factor is greater than 20. Usually this range varies from 20 to 500.

RELATION BETWEEN β AND α

$$\beta = \frac{\Delta I_C}{\Delta I_B}$$

$$\alpha = \frac{\Delta I_C}{\Delta I_E}$$

$$I_E = I_B + I_C$$

$$\Delta I_E = \Delta I_B + \Delta I_C$$

$$\Delta I_B = \Delta I_E - \Delta I_C$$

$$\beta = \frac{\Delta I_C}{\Delta I_E - \Delta I_C}$$

$$\beta = \frac{\Delta I_C / \Delta I_E}{\frac{\Delta I_E}{\Delta I_E} - \frac{\Delta I_C}{\Delta I_E}} = \frac{\alpha}{1 - \alpha}$$

$$\beta = \frac{\alpha}{1 - \alpha}$$

EXPRESSION FOR COLLECTOR CURRENT

$$I_C = \alpha I_E + I_{CBO}$$

$$I_E = I_B + I_C = I_B + (\alpha I_E + I_{CBO})$$


$$I_E (1 - \alpha) = I_B + I_{CBO}$$

$$I_E = \frac{I_B}{1 - \alpha} + \frac{I_{CBO}}{1 - \alpha}$$

$$I_C ; I_E = *(\beta + 1) I_B + (\beta + 1) I_{CBO}$$

CHARACTERISTICS OF COMMON EMITTER CONFIGURATION

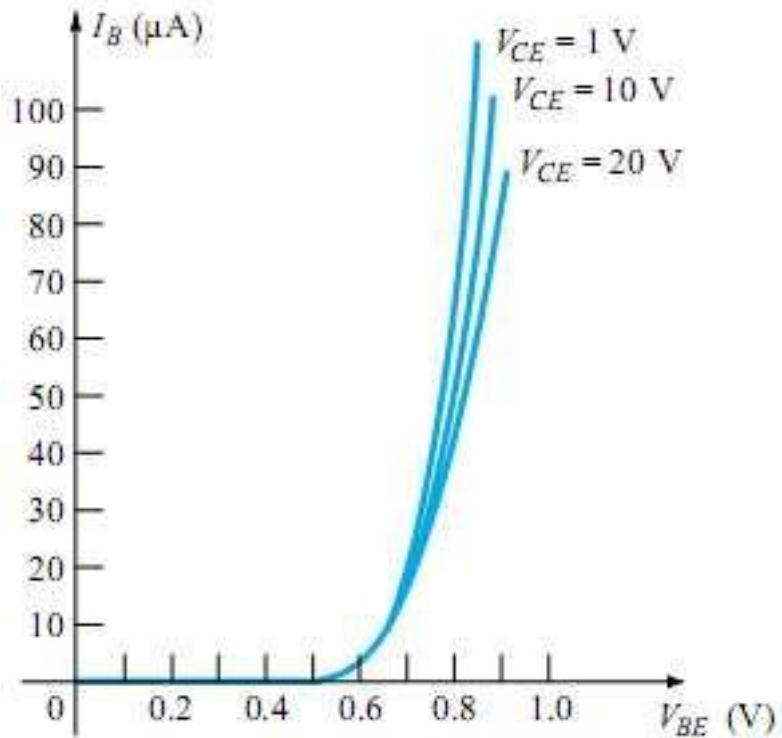- Input Characteristics: $\rightarrow V_{BE}$ vs I_B characteristics is



called input characteristics.


$\rightarrow I_B$ increases rapidly with V_{BE} . It means input resistance is very small.

$\rightarrow I_E$ almost independent of V_{CE} .

$\rightarrow I_B$ is of the range of micro amps.

CHARACTERISTICS OF COMMON EMITTER CONFIGURATION

- Output Characteristics:

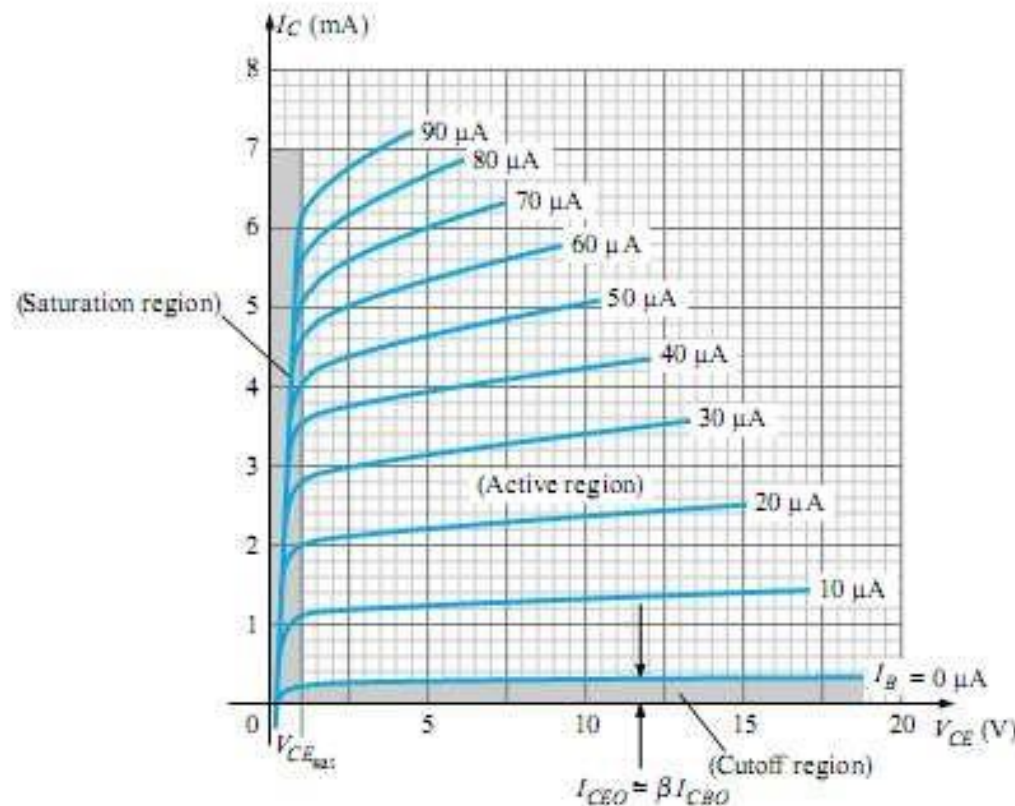

- V_{CE} vs I_C characteristics is called output characteristics.
- I_C varies linearly with V_{CE} , only when V_{CE} is very small.
- As, V_{CE} increases, I_C becomes constant.

EXPRESSION FOR COLLECTOR CURRENT

$$I_C = \alpha I_E + I_{CBO}$$

$$I_E = I_B + I_C = I_B + (\alpha I_E + I_{CBO})$$

$$I_E (1 - \alpha) = I_B + I_{CBO}$$

$$I_E = \frac{I_B}{1 - \alpha} + \frac{I_{CBO}}{1 - \alpha}$$

$$I_C ; I_E = *(\beta + 1) I_B + (\beta + 1) I_{CBO}$$

$$\beta = \frac{\alpha}{1 - \alpha} \quad \therefore \quad \beta + 1 = \frac{\alpha}{1 - \alpha} + 1 = \frac{1}{1 - \alpha}$$


COMPARISON OF TRANSISTOR CONNECTION

S. No.	Characteristic	Common base	Common emitter	Common collector
1.	Input resistance	Low (about 100 Ω)	Low (about 750 Ω)	Very high (about 750 k Ω)
2.	Output resistance	Very high (about 450 k Ω)	High (about 45 k Ω)	Low (about 50 Ω)
3.	Voltage gain	about 150	about 500	less than 1
4.	Applications	For high frequency applications	For audio frequency applications	For impedance matching
5.	Current gain	No (less than 1)	High (β)	Appreciable

TRANSISTOR LOAD LINE ANALYSIS

- In transistor circuit analysis it is necessary to determine collector current for various V_{CE} voltage.
- One method is we can determine the collector current at any desired V_{CE} voltage, from the output characteristics.
- More conveniently we can use load line analysis to determine operating point.

TRANSISTOR LOAD LINE ANALYSIS

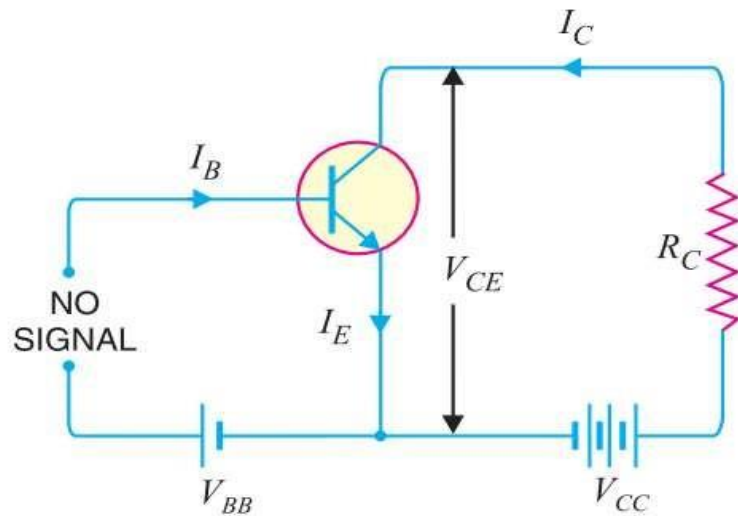

- Consider common emitter npn transistor ckt shown in figure.
- There is no input signal.
- Apply KVL in the output ckt-

$$V_{CE} = V_{CC} - I_C R_C$$

(i) When the collector current $I_C = 0$, then collector-emitter voltage is maximum and is equal to V_{CC} i.e.



$$\begin{aligned} \text{Max. } V_{CE} &= V_{CC} - I_C R_C \\ &= V_{CC} \quad (\because I_C = 0) \end{aligned}$$

When collector-emitter voltage $V_{CE} = 0$,

$$\begin{aligned} V_{CE} &= V_{CC} - I_C R_C \\ 0 &= V_{CC} - I_C R_C \end{aligned}$$

$$\text{Max. } I_C = V_{CC} / R_C$$

TRANSISTOR LOAD LINE ANALYSIS

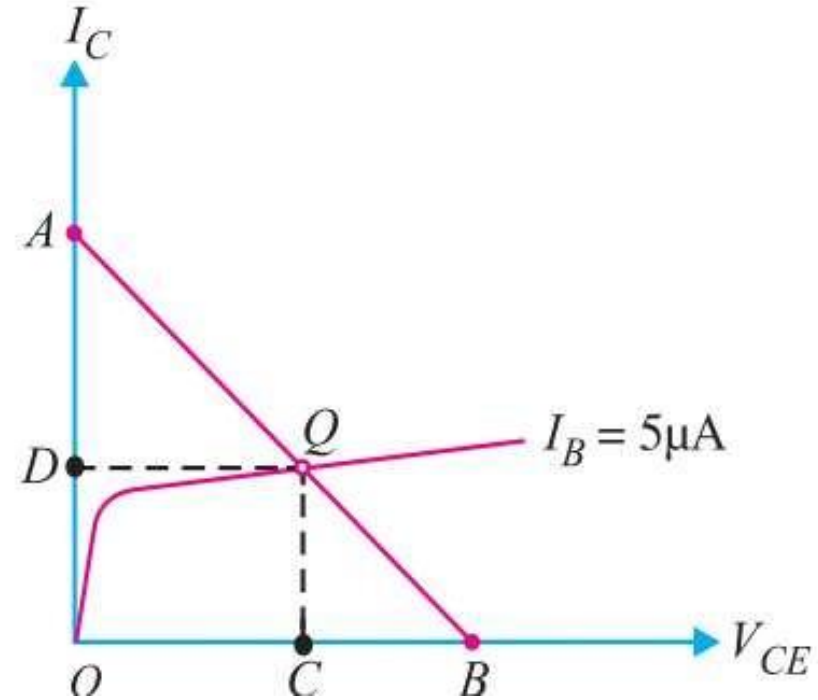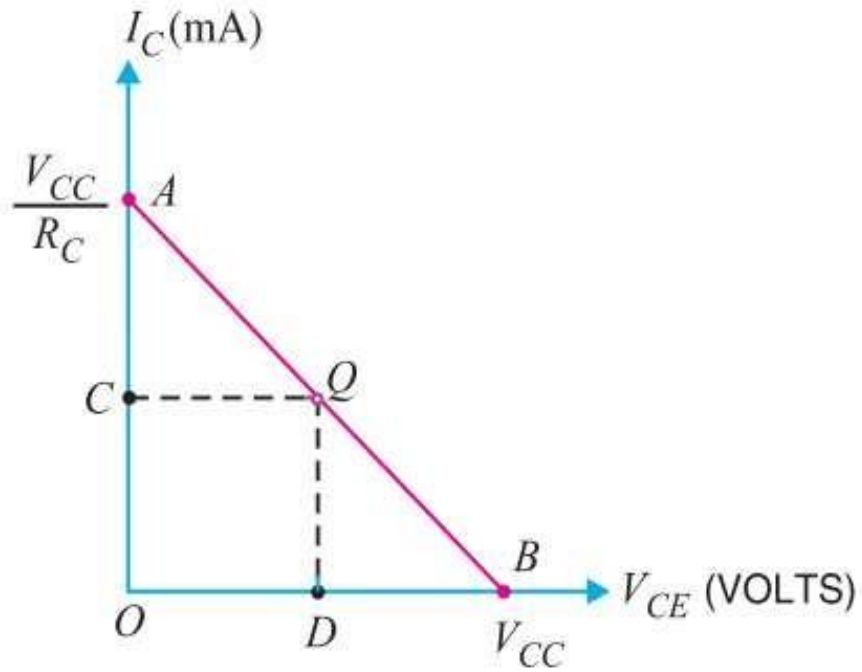

OPERATING POINT

*The zero signal values of I_C and V_{CE} are known as the **operating point**.*

- It is called operating point because variation of I_C takes place about this point.
- It is also called quiescent point or Q-point.

