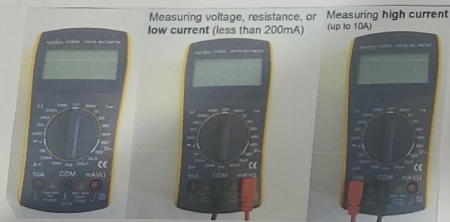


# Index

S. No.	Name of the Experiment	Page No.	Date of Experiment	Date of Submission	Remarks
1	Exp-1 > Intro to lab	1-2	4/02/25		
2	Exp-2 > V-I relation in Diode	3-5	11/2/25		
3	Exp-3 > Amplifier Circuit using OPAMP 741	6-8	19/2/25		
4	Exp-4 > LOGIC GATES	9-10	22/2/25		
5	Exp-5 > Implementation using NAND Gate	11-12	26/2/25		



Dual Power Supply



Measuring voltage, resistance, or low current (less than 200mA) Measuring high current (up to 10A)

## Experiment - 1

Aim - To introduce the electronics laboratory and familiarize students with basic equipments and components used in experiment.

## Theory -

1. Cathode Ray Oscilloscope (CRO): Displays electrical signals as waveforms on a screen using a cathode-ray-tube (CRT). Measures peak voltage, frequencies and phase differences.
2. Function Generator: Generates waveforms like sine, square & triangle over a wide frequency range for testing circuits.
3. Dual DC power supply: Provides adjustable DC voltage & current (max 2A) with constant current / voltage modes & overload protection.
4. Digital Multimeter (DMM): Measures AC/DC voltage, currents, resistance and tests diodes / continuity. Displays readings on LCD.

Teacher's Signature \_\_\_\_\_



4-Band Code

2%, 5%, 10% 500Ω ± 5%

COLOR	1 <sup>st</sup> BAND	2 <sup>nd</sup> BAND	3 <sup>rd</sup> BAND	MULTIPLIER	TOLERANCE
Black	0	0	0	10	± 1% (F)
Brown	1	1	1	100	± 1% (G)
Red	2	2	2	1000	± 2% (J)
Orange	3	3	3	10K	
Yellow	4	4	4	100K	
Green	5	5	5	1M	± 0.5% (B)
Blue	6	6	6	10M	± 0.25% (C)
Violet	7	7	7	100M	± 0.15% (D)
Grey	8	8	8	1000M	± 0.05% (E)
White	9	9	9	1G	
Gold				0.10	± 5% (I)
Silver				0.010	± 10% (K)

5-Band Code

0.1%, 0.25%, 0.5%, 1% 237Ω ± 1%

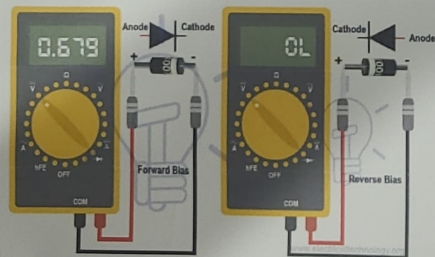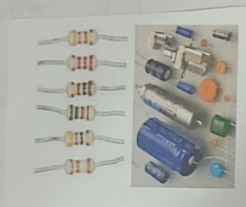

5. Resistors:- Resist current flow, measured in ohm ( $\Omega$ ). Values are identified by colour codes.

6. Capacitors:- Stores energy in a electric field b/w 2 plates separated by a dielectric.

7. Diodes:- Allow current in forward bias and block in reverse bias.

8. Transistors:- Three terminal devices that amplify or switch currents using a small base current.

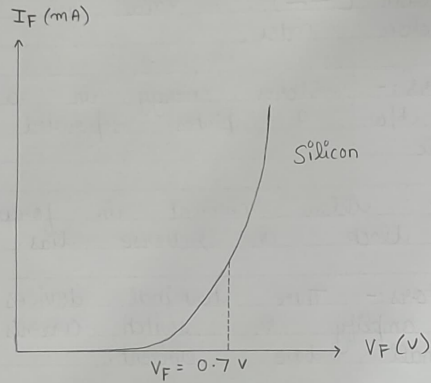


Fig-1) Forward Bias of Si Diode

## Experiment - 2

**Aim -** To see Voltage Current relations in Diodes by applying a voltage across it & measure the corresponding current flowing through it.

**Apparatus Required -**

- Diode
- A DC Voltage supply
- Bread Board
- 1 K- $\Omega$  resistor
- 2 multimeters for measuring current & voltage
- Connecting Wires.

**Theory -** A Diode is a device formed from n-type & p-type semiconductor material. The lead connected to the p-type material is called anode & lead connected to n-type material is cathode. In general cathode of diode is marked by solid line on diode. Primary function of diode is rectification. When it is forward bias it pass current & blocks in reverse bias. A general curve looks like this. (Fig - 1)



In the forward bias region the V-I relationship is described as follows:

$$I = I_s (e^{V/mV_T} - 1)$$

$I \Rightarrow$  Forward Current

$V \Rightarrow$  Forward Voltage

$V_T = kT/q \Rightarrow$  Thermal Voltage.

Initially V vs I Graph is linear but then after reaching breakdown, it becomes exponential.

Procedure - First complete a circuit as shown in figure below with a  $1\text{ K}\Omega$  resistor & a variable DC input voltage source.

We first note the point where ammeter starts deflecting, we note this point & gradually increase the input voltage & take the corresponding current readings. Now change direction of voltage & get readings in reverse bias.


## Result

Supply Voltage	$V_D$	$I_D$	$V_R$
0.7 V	0.509 V		
1.0 V	0.555 V		
1.5 V	0.585 V		
1.6 V	0.592 V		
2.0 V	0.605 V		
2.5 V	0.621 V		
3.0 V	0.632 V		
3.5 V	0.640 V		


## Precautions:

- Connections should be done carefully
- Readings shall be noted carefully.
- Proper connection.

## Inverting Amplifier

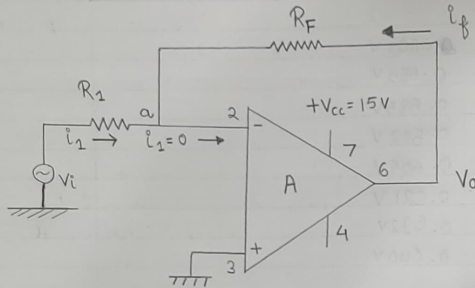

## Input & Output Waveforms

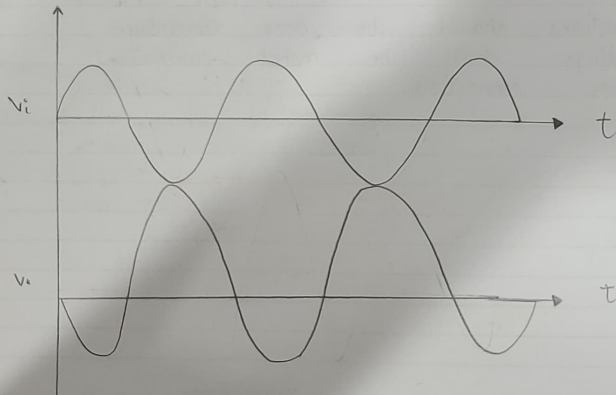

Expt. No. 3

Date 19/2/25

Page No. 6

## Experiment - 3

Aim - To design an inverting & non inverting amplifier circuit using OPAMP 741.

Equipment - CRO, Function generator, power supply, Multimeter, Bread Board & CRO probes.

## Theory

→ Inverting Amplifier: The inverter is the basic building block of any circuit. The circuit is shown in figure.  $V_o$  is output voltage & its feedback to the inverting input terminal through  $R_F$  &  $R_1$  network.



Input signal  $V_i$  (ac) is applied to inverting input terminal via  $R_1$  & non inverting input terminal is grounded.

Assume an Ideal Op Amp. As  $V_1 = 0$ , node a is at virtual Ground potential. Nodal eq<sup>n</sup> at point a yields.

$$i_i + i_f = 0, \quad \frac{V_i}{R_1} + \frac{V_o}{R_F} = 0$$

$$V_o = -\frac{R_F}{R_1} V_i$$

Teacher's Signature \_\_\_\_\_

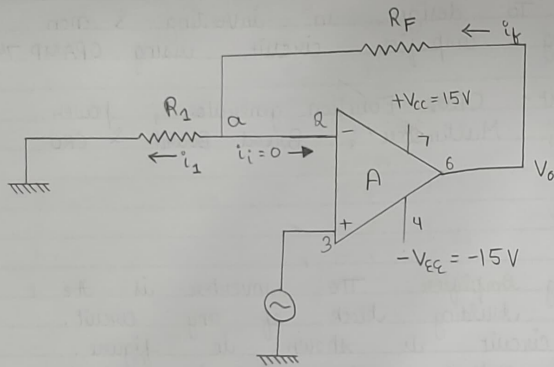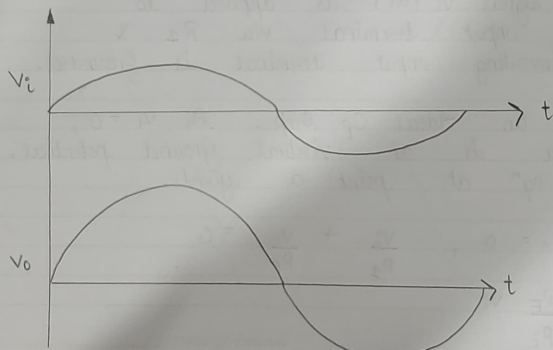Non-inverting AmplifierInput & Output Waveforms

⇒ Non-inverting Amplifier:- When ac is applied and circuit provides input signal without inverting it, such a circuit is called non-inverting amplifier.

As  $V_d$  at input terminal of Op Amp is zero, voltage at node 'a' is  $V_i$ , same as input voltage applied to non-inverting input terminal.  $R_F$  &  $R_1$  forms a potential divider.

$$i_1 = i_F, \quad \frac{V_i}{R_1} = \frac{V_o - V_i}{R_F}, \quad \frac{V_i}{R_1} + \frac{V_i}{R_F} = \frac{V_o}{R_F}$$

$$V_o = \left\{ 1 + \frac{R_F}{R_1} \right\} V_i$$

Observations(i) Inverting Amplifiers

S.no	Resistors		Input		Output Voltage	Gain
	$R_L$	$R_F$	Voltage	Freq		
1.	1K $\Omega$	10K $\Omega$	10 mV	1KHz	-100 mV	-10
2.	1K $\Omega$	10K $\Omega$	20 mV	1KHz	-200 mV	-10
3.	1K $\Omega$	10K $\Omega$	30 mV	1KHz	-300 mV	-10
4.	1K $\Omega$	10K $\Omega$	40 mV	1KHz	-400 mV	-10
5.	1K $\Omega$	10K $\Omega$	50 mV	1KHz	-500 mV	-10
6.	1K $\Omega$	10K $\Omega$	60 mV	1KHz	-600 mV	-10
7.	1K $\Omega$	10K $\Omega$	70 mV	1KHz	-700 mV	-10

Teacher's Signature \_\_\_\_\_



## (ii) Non-Inverting Amplifier

S.no	Resistors		Input		Output	Gain
	$R_L$	$R_F$	Voltage	Frequency	Voltage	
1	1K $\Omega$	10K $\Omega$	10 mV		110 mV	+11
2	1K $\Omega$	10K $\Omega$	20 mV		220 mV	+11
3	1K $\Omega$	10K $\Omega$	30 mV		330 mV	+11
4	1K $\Omega$	10K $\Omega$	40 mV		440 mV	+11
5	1K $\Omega$	10K $\Omega$	50 mV		550 mV	+11
6	1K $\Omega$	10K $\Omega$	60 mV		660 mV	+11
7	1K $\Omega$	10K $\Omega$	70 mV		770 mV	+11

Calculations & Result:

$$R_1 = 1K\Omega \text{ \& } R_F = 10K\Omega \left\{ \text{Inverting Amplifier} \right\}$$

$$\text{Gain} = -10$$

$$R_2 = 1K\Omega \text{ \& } R_F = 10K\Omega \left\{ \text{Non Inverting Amplifier} \right\}$$



$$\text{Gain} = 11$$

Precautions -

- All connections should be done carefully
- Avoid excessive input signals
- Ensure proper polarity

Conclusion- The experiment successfully demonstrates the functionality of both inverting & non inverting amplifier using an OPAMP 741.

Teacher's Signature \_\_\_\_\_

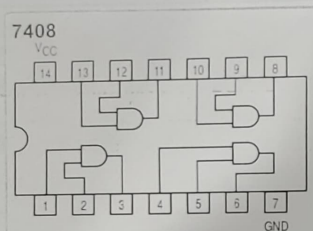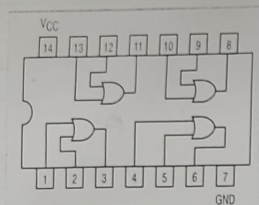

Expt. No. 4

Date 22/2/25

Page No. 9

## Experiment - 4

**Aim** - To verify the truth tables of logic gates (OR, AND, NOT, NAND, NOR, XOR), using their respective ICs.

**Apparatus** - Logic Gate ICs (eg:- 7400 for NAND), Breadboard, Connecting wires, Power supply, Push Buttons.

**Procedure & Table :-**




### OR GATE - Truth Table

Input		Output
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

### AND GATE - Truth Table

Input		Output
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

Teacher's Signature \_\_\_\_\_

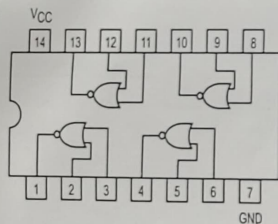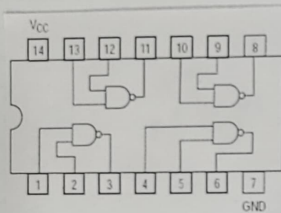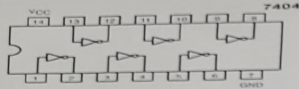

Expt. No. 4

Date 22/2/25

Page No. 10

### NAND GATE - Truth Table

Input		Output
A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


### NOR Gate - Truth Table

Input		Output
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

### XOR Gate - Truth Table

Input		Output
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

Teacher's Signature \_\_\_\_\_

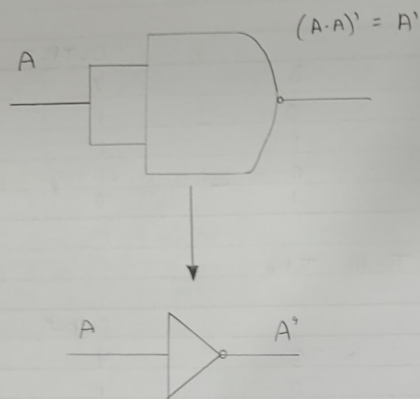

Implementing NOT gate using NAND gate

### Experiment - 5

**Aim:-** Design & implementation using NAND Gate

**Apparatus:-** Connecting Wires, Gates, Breadboard & Power Supply

**Theory:-** AND, OR, NOT is called basic gates as their logical operation cannot be simplified further. NAND & NOR gates are called universal gates as using only NAND or only NOR, any logic function can be implemented. Using NAND or NOR gates & De Morgan's Theorems, different basic gates & Ex-or gates are realized.



i) Implementing NOT gate using NAND gate

The figure shows 2 ways in which a NAND gate can be used as an inverter (NOT gate).



- 1) All NAND input pins connect to the input signal A gives an output.
- 2) One NAND input pin is connected to input signal A, while others to logic 1. Output will be  $A'$ .



Implementing AND gate using NAND gate.

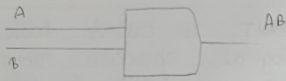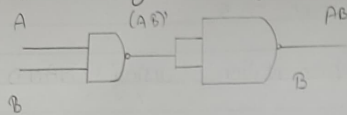

Implementing OR gate using NAND gate

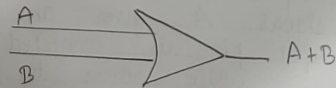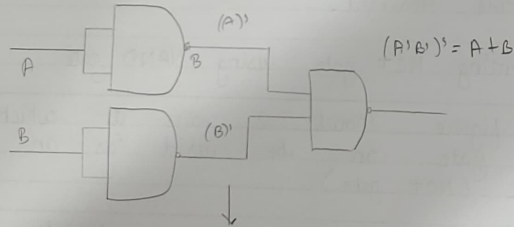

ii) Implementing AND gate using NAND gate

An AND gate can be replaced by a NAND gates as shown in figure.

iii) Implementing OR gate using NAND gate

An OR gate can be replaced by NAND gates as shown in figure.

Result :- Using the procedures mentioned before, we can use NAND gate.