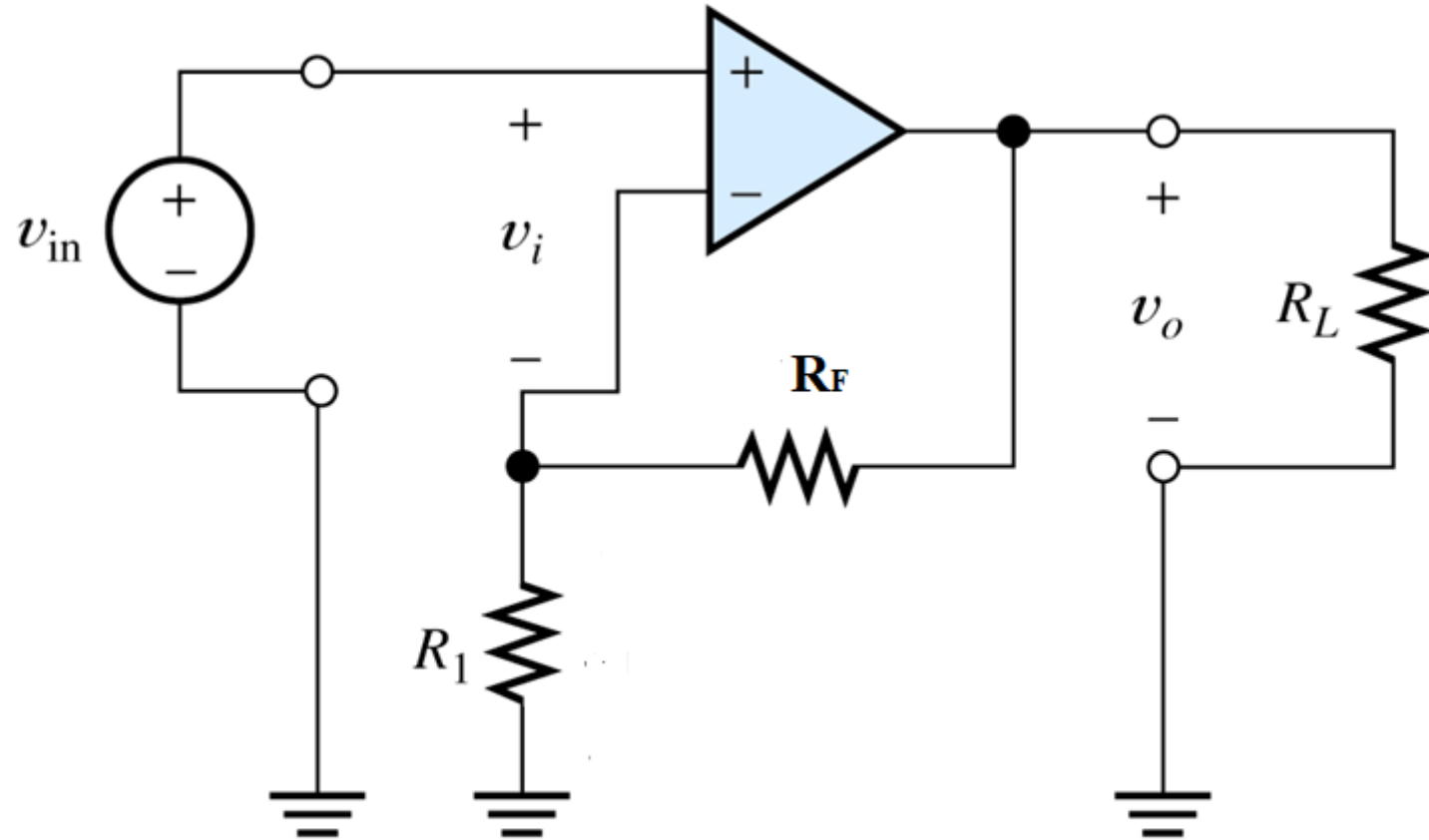


# **OPERATIONAL AMPLIFIER (OP-AMP)**


# NON-INVERTING AMPLIFIER



# NON-INVERTING AMPLIFIER

- Input is applied to non-inverting terminal
- Feedback is given to inverting terminal
- Output voltage will be in-phase with input voltage
- Here again, the following assumptions are made
  - Since  $A_d$  is very high,  $v_{id}$  should be very small;  $v_{id}$  taken as almost zero
  - Current entering OPAMP input terminal is almost zero

# NON-INVERTING AMPLIFIER

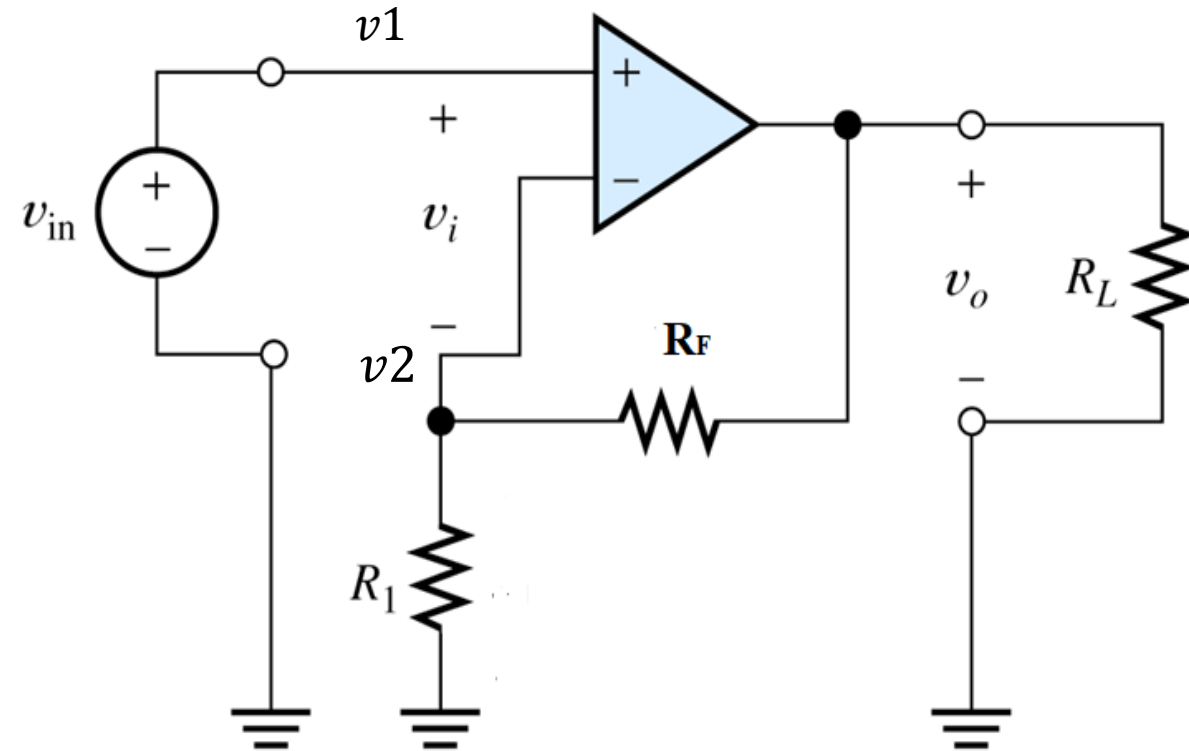

# NON-INVERTING AMPLIFIER

$$v_{id} = 0$$

$$v_1 = v_2 = v_{in}$$


$$i_1 = \frac{v_2}{R_1} = \frac{v_{in}}{R_1}$$

$$i_2 = \frac{v_o - v_2}{R_F} = \frac{v_o - v_{in}}{R_F}$$

$$i_1 = i_2$$

$$\frac{v_{in}}{R_1} = \frac{v_o - v_{in}}{R_F}$$
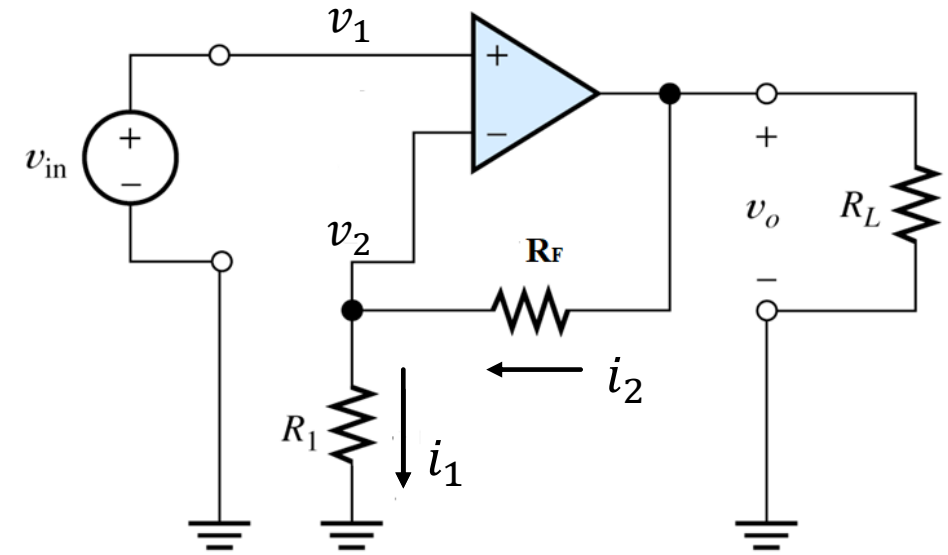
$$v_o = v_{in} \left( 1 + \frac{R_F}{R_1} \right)$$




## PROBLEMS

1. For an non-inverting amplifier using OPAMP,  $R_1=1K$ ,  $R_F=100K$ ,  $v_{in}=0.1\sin(\omega t)$ . Find  $v_o$ .
2. For a non-inverting amplifier,  $R_1=10K$ ,  $R_F=100K$ . Calculate  $v_o$  if  $v_i = 25$  mV dc.
3. An ac signal of rms value 2 mV needs to be amplified to 1.2 V rms, and output must be in same phase as input. Design a suitable amplifier choosing  $R_1=2K$

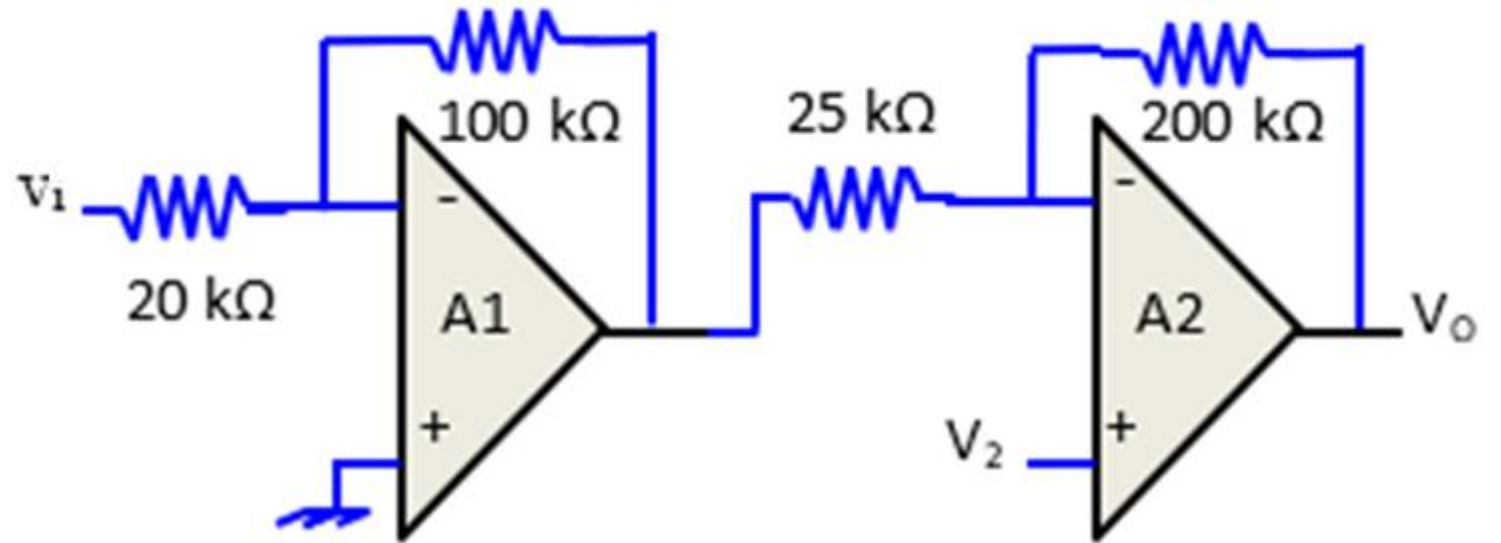
## EXAMPLE 4

Find the output voltage  $V_O$  for the following circuit if  $v_1 = 2\text{V} = V_2$ .


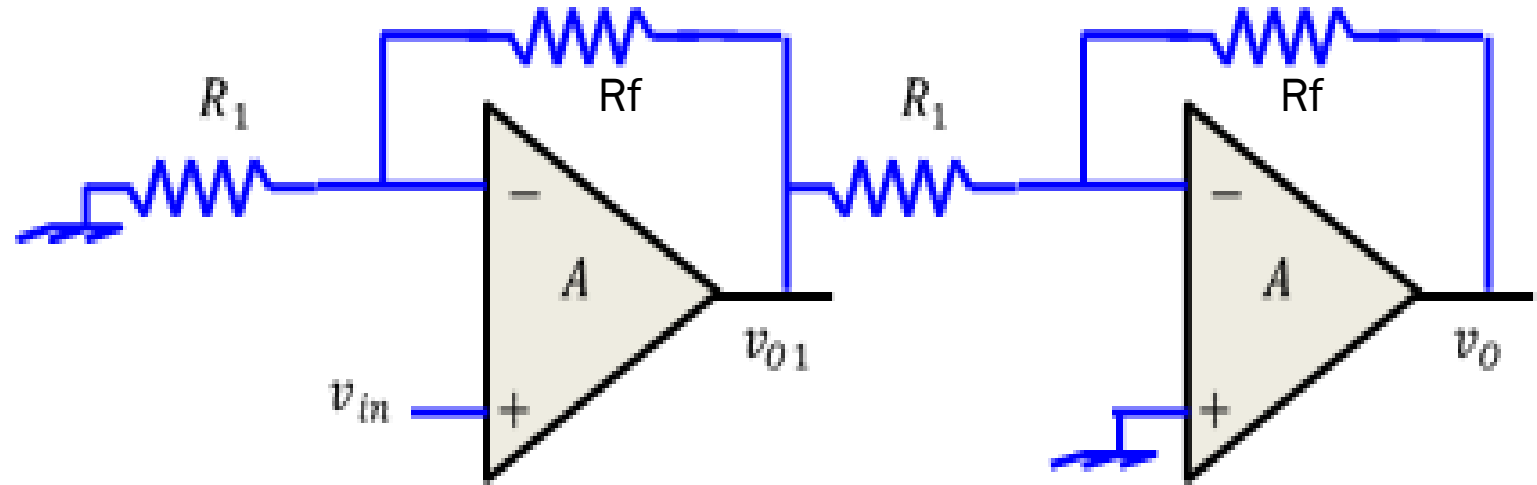
## EXAMPLE 5


Find the output voltage  $V_O$  for the following circuit if  $V_{in} = 2V$ ,  $R_1 = 2k$  and  $R_f = 10k$ .





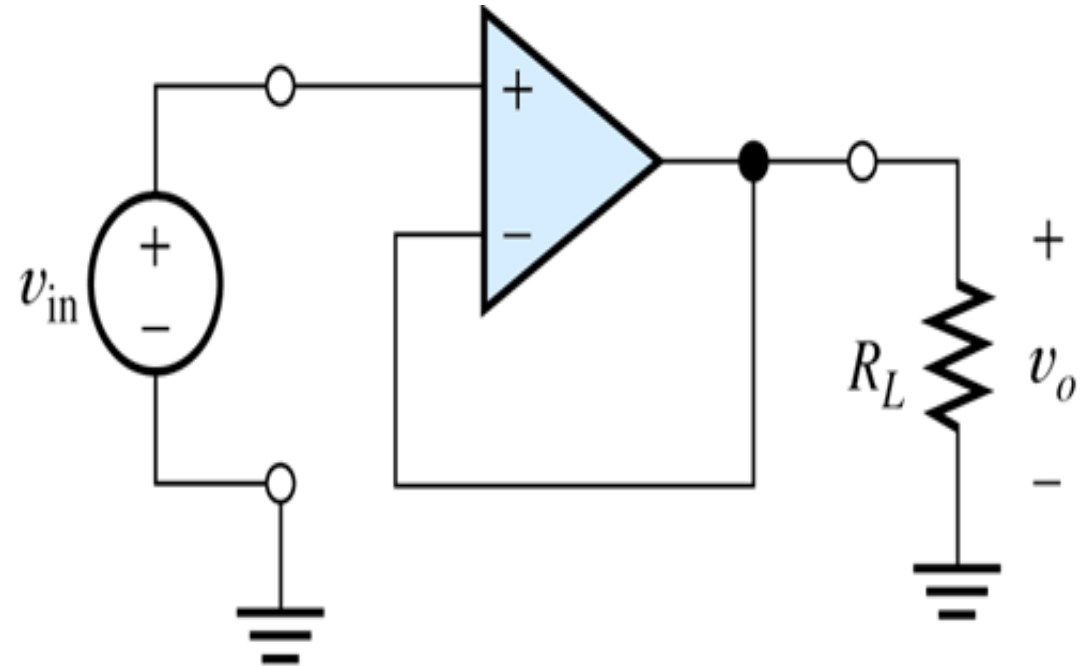
## VOLTAGE FOLLOWER

- Special case of non-inverting amplifier where  $R_F=0$
- Voltage gain is unity.  $v_o = v_{in}$
- Has very high input resistance and very low output resistance; Used as buffer for impedance matching



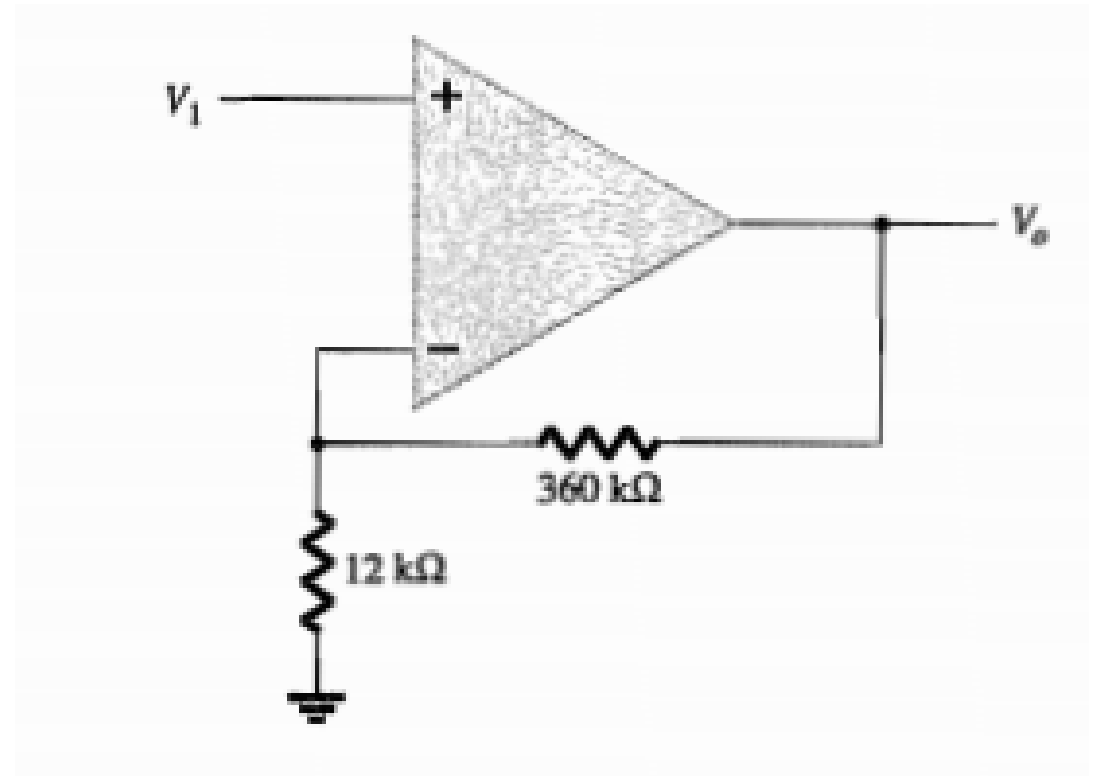
## EXAMPLE 6

Find the output voltage  $V_0$  for the following circuit if  $v_1 = 2\text{V} = V_2$ .



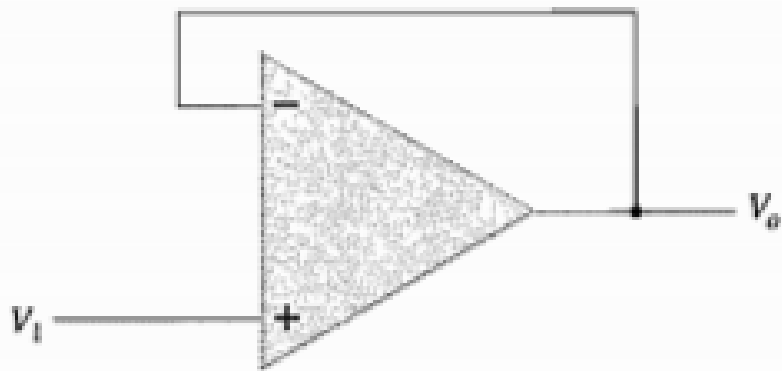
## EXAMPLE 7

Find the output voltage  $V_o$  for the following circuit if  $v_1 = 2\text{ V}$ .




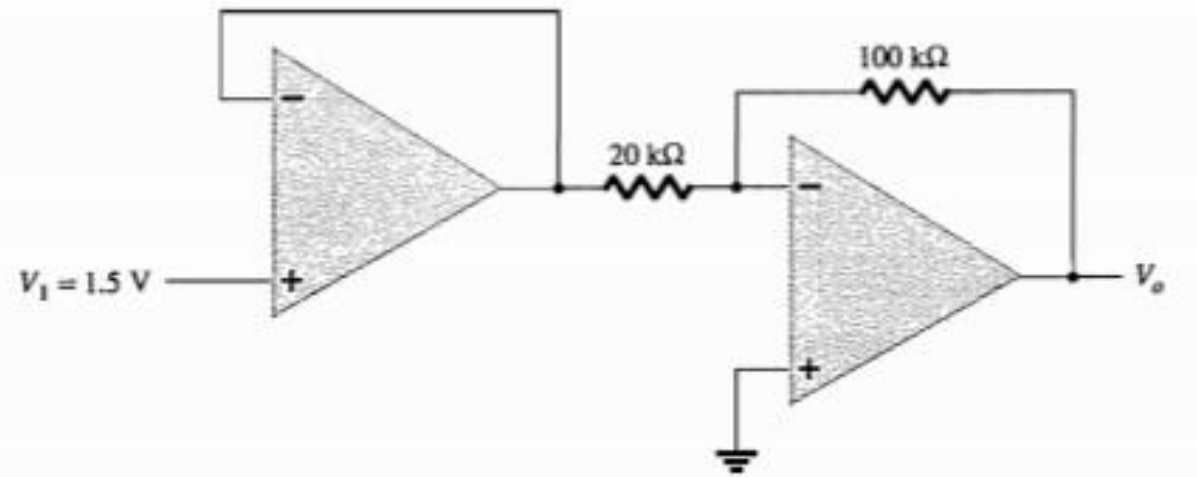Find the output voltage  $V_o$  for the following circuit.


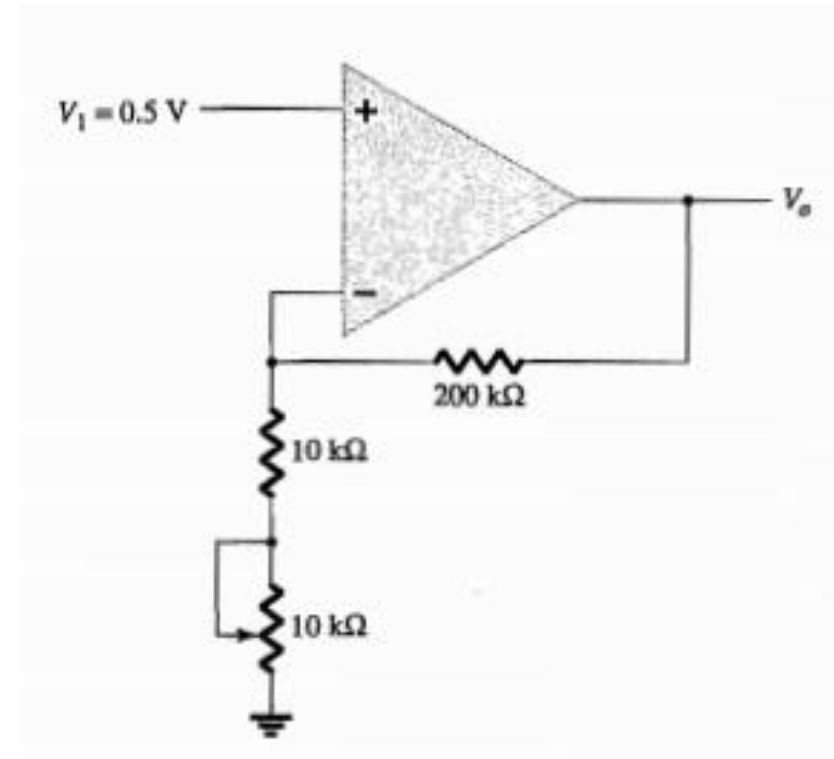
## EXAMPLE 8

Calculate the range of output voltage for the circuit.



■ Thank You