



**MANIPAL UNIVERSITY  
JAIPUR**

*(University under Section 2(f) of the UGC Act)*



# B.TECH FIRST YEAR

ACADEMIC YEAR: 2023-2024



## COURSE NAME: EES

COURSE CODE : EE 1002

LECTURE SERIES NO :

CREDITS : 4

MODE OF DELIVERY : (POWER POINT PRESENTATION)

FACULTY

EMAIL-ID

PROPOSED DATE OF DELIVERY:



**MANIPAL UNIVERSITY  
JAIPUR**

### VISION

Global Leadership in Higher Education and Human Development

### MISSION

- Be the most preferred University for innovative and interdisciplinary learning
- Foster academic, research and professional excellence in all domains
- Transform young minds into competent professionals with good human values


### VALUES

Integrity, Transparency, Quality,  
Team Work, Execution with Passion, Humane Touch

# OPERATIONAL AMPLIFIER (OP- AMP)

## Reference Book:

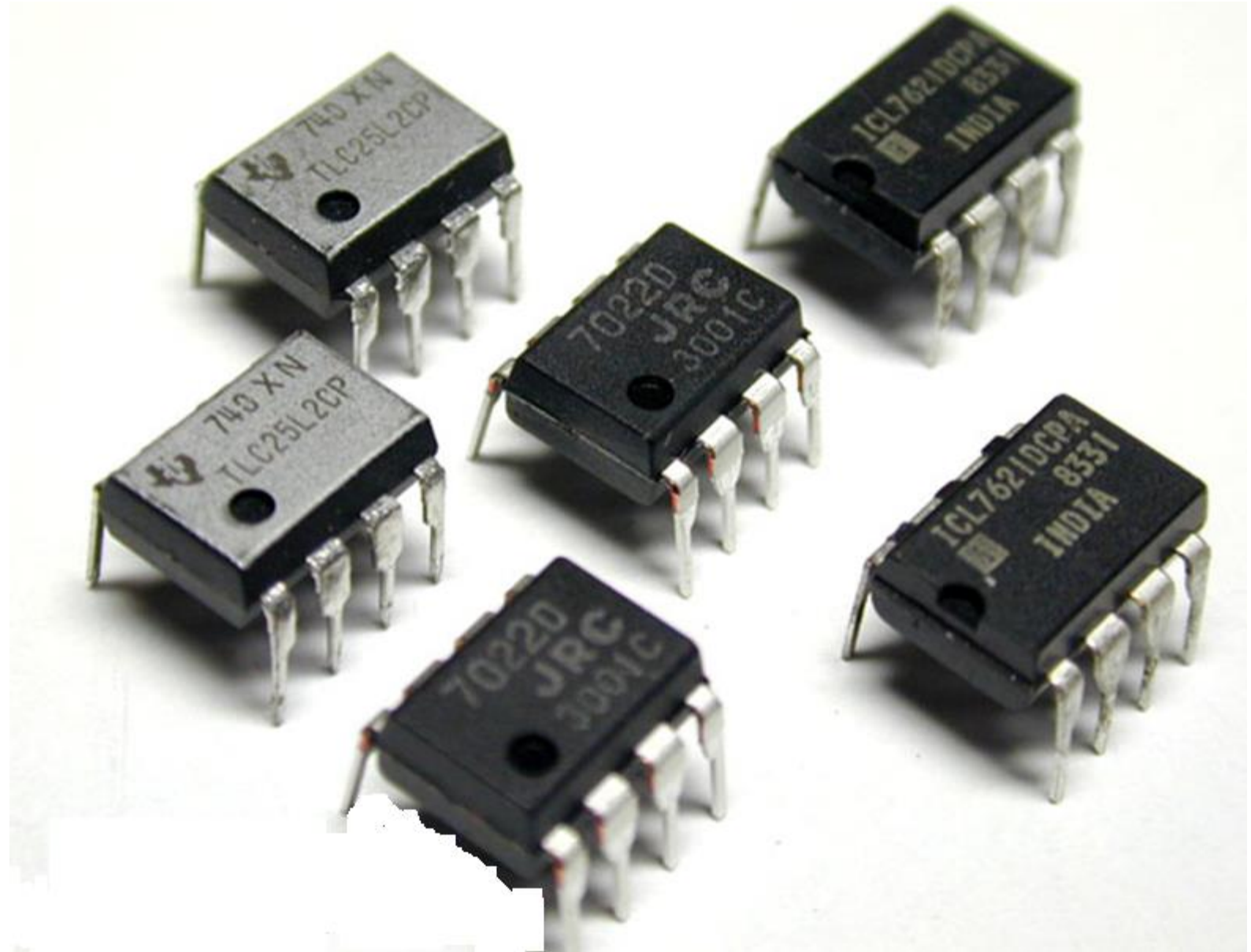- 1. OPAMPS and Linear Integrated Circuits  
by Ramakanth Gayakwad



---

# CONTENTS

- Introduction
- OPAMP Symbol
- Internal block diagram
- Open-loop configuration
- Common mode rejection ratio
- OPAMP equivalent circuit
- OPAMP characteristics


# INTRODUCTION

- Operational Amplifier (OPAMP) is a direct coupled high-gain amplifier fabricated on Integrated Circuit (IC)
- Op-amps are linear devices that are ideal for DC and AC amplification and are used often in signal conditioning, filtering .
- Earlier, op-amp were used primarily to perform mathematical operation such as summation, subtraction, differentiation and integration etc. so named as op-amp.
- Typical application of op-amp includes –
  1. Audio amplifier-voltage amplitude change
  2. Signal generators- oscillators,
  3. Signal filter circuits
  4. Instrumentation circuits---Biomedical Instrumentation

# INTRODUCTION

- Advantages of OP-AMP over transistor amplifier
  - Less power consumption
  - Costs less
  - More compact, fabricated in a single chip.
  - More reliable
  - Higher gain can be obtained
  - Easy design

# OPAMP TERMINALS

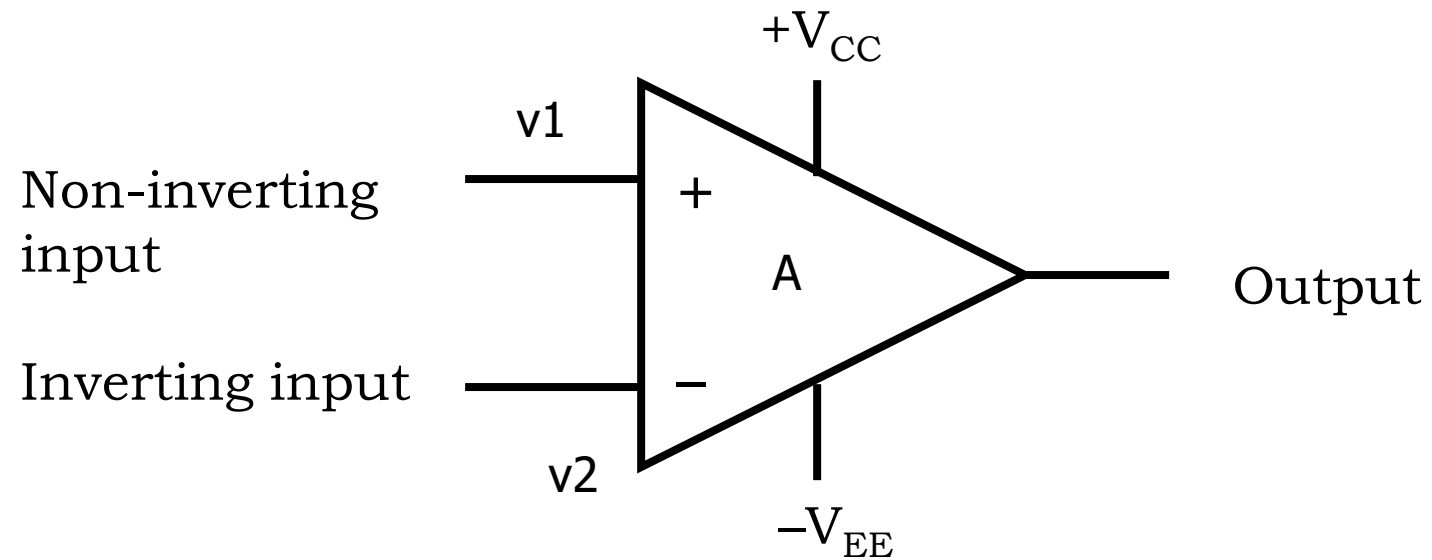

Here,  $A$  = Large signal voltage gain


---

## OP-AMP TERMINALS

- If input is applied to non-inverting input terminal, then output will be in-phase with input
- If input is applied to inverting input terminal, then output will be 180 degrees out of phase with input
- If inputs are applied to both terminals, then output will be proportional to difference between the two inputs

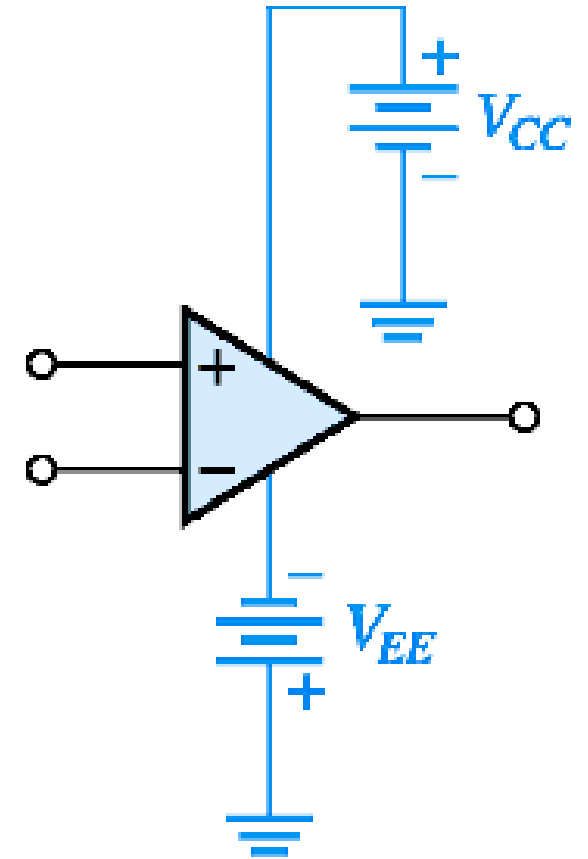
## OPAMP TERMINALS

- Two DC power supplies (dual) are required
- Magnitudes of both may be same
- The other terminal of both power supplies are connected to common ground
- All input and output voltages are measured with reference to the common ground






# OPAMP TERMINALS

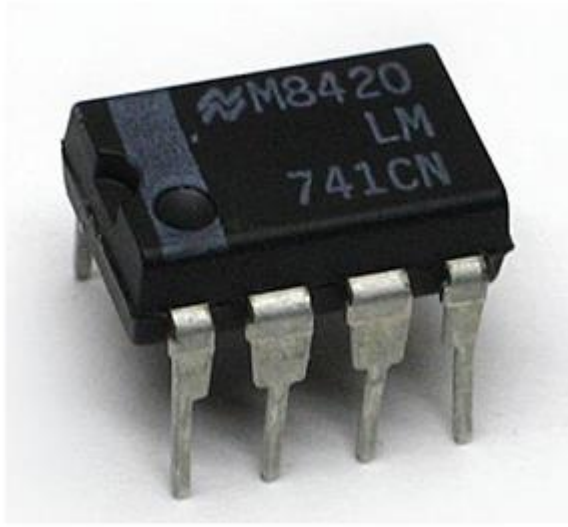

Integrated Circuit

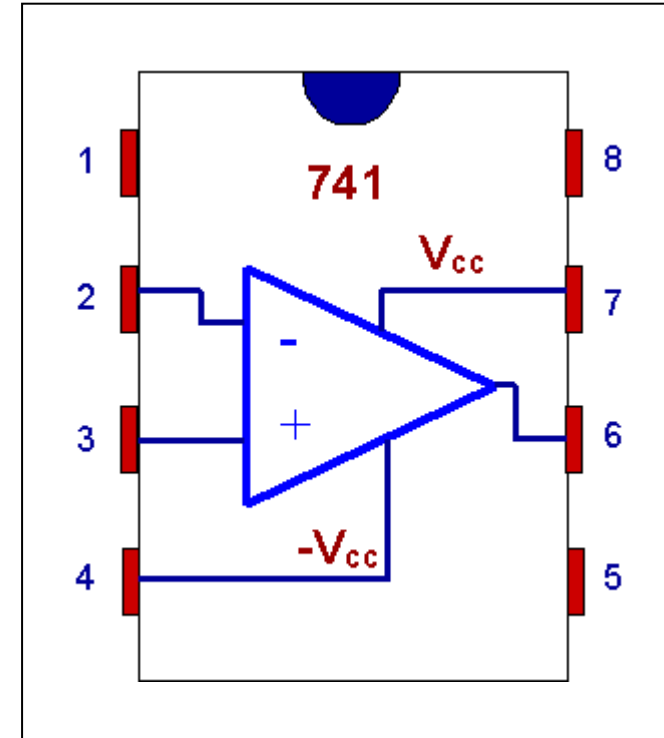
- Pin 1 & 5 Offset null
- Pin 2 & 3 input
- Pin 4 & 7 VCC



Pin Diagram

- |       |               |
|-------|---------------|
| Pin 6 | Output        |
| Pin 8 | Not connected |

# INTERNAL BLOCK DIAGRAM

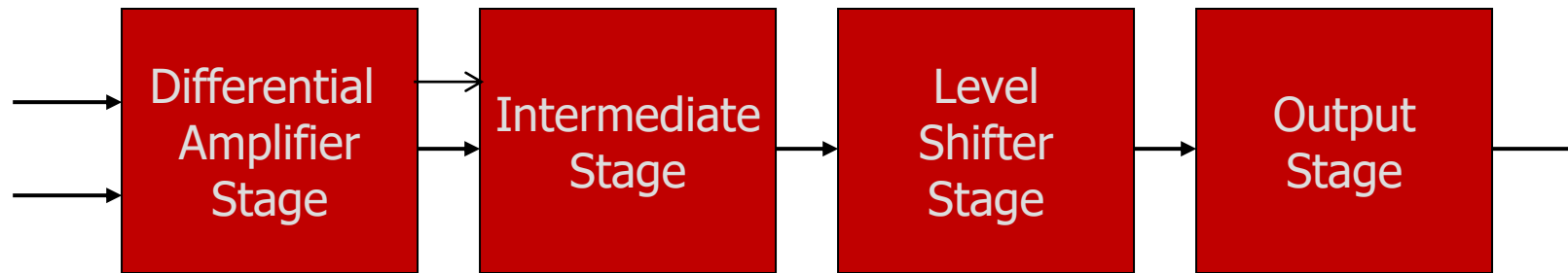

Dual input,  
Balanced output  
Differential amplifier

Dual input  
unbalanced output  
Differential amplifier

Such as  
emitter follower  
Using constant  
current source


Complementary  
symmetry  
push-pull amplifier

## INTERNAL BLOCK DIAGRAM

Four stages can be identified –

- Input stage or differential amplifier stage can amplify difference between two input signals; Input resistance is very high; Draws zero current from the input sources
- Intermediate stage (or stages) use direct coupling; provide very high gain
- Level shifter stage shifts the dc level of output voltage to zero (can be adjusted manually using two additional terminals)
- Output stage is a power amplifier stage; has very small output resistance; so output voltage is the same, no matter what is the value of load resistance connected to the output terminal

## OPEN-LOOP CONFIGURATION

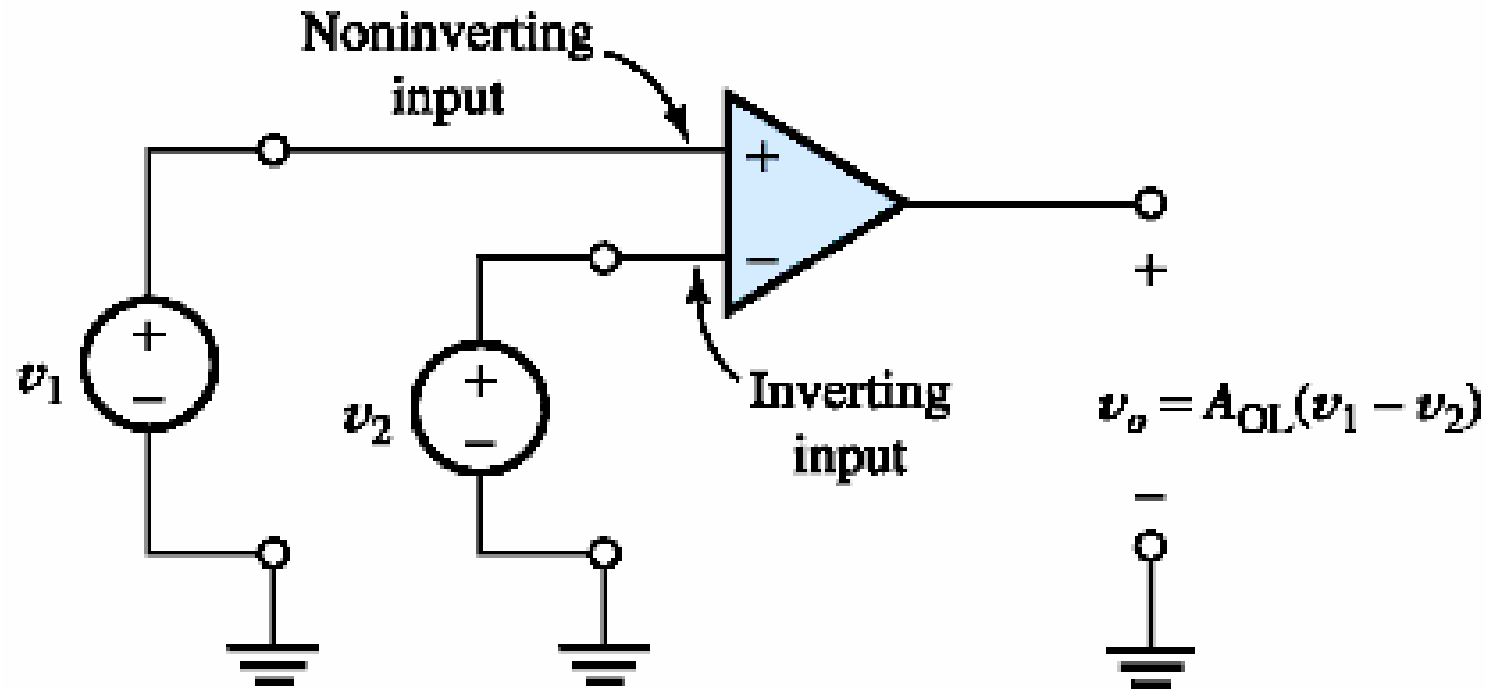

If  $v_1 = 0$ , then  $v_o = -A_{OL}v_2$  Inverting amplifier

If  $v_2 = 0$ , then  $v_o = A_{OL}v_1$  Non-inverting amp

## OPEN-LOOP CONFIGURATION

- $A_{OL}$  is the open-loop voltage gain of OPAMP  
Its value is very high  
Typical value is 0.5 million
- So, even if input is in micro volts, output will be in volts
- But output voltage cannot cross the value of power supply  $V_{CC}$
- So, if input is in milli volts, output reaches saturation value  $V_{sat} = V_{CC}$  (or  $V_{EE}$ )

## OPEN-LOOP CONFIGURATION

- If  $v_1 = v_2$ , then ideally output should be zero
- But in practical Op-Amp, output is

$$v_o = A_{cm} \left( \frac{v_1 + v_2}{2} \right)$$

Where,  $A_{CM}$  is the common-mode gain of Op-Amp

- So, final gain equation is:

$$v_o = A_d (v_1 - v_2) + A_{cm} \left( \frac{v_1 + v_2}{2} \right)$$

$$v_o = A_d v_{id} + A_{cm} v_{icm}$$

## OPEN-LOOP CONFIGURATION

- Common-mode rejection ratio
  - It is a measure of the ability of Op-Amp to reject the signals common to both input terminals (noise)
  - Defined as

$$CMRR = \frac{A_d}{A_{cm}}$$

$$(CMRR)_{dB} = 20 \log_{10} \left( \frac{A_d}{A_{cm}} \right)$$

## PROBLEMS

- An OPAMP has differential voltage gain of 100,000 and CMRR of 60 dB. If non inverting input voltage is  $150\text{ }\mu\text{V}$  and inverting input voltage is  $140\text{ }\mu\text{V}$ , calculate the output voltage of OPAMP

Ans: 1.01 V


- For an OPAMP, when  $v_1$  is 0.5 mV and  $v_2$  is  $-0.5\text{ mV}$ , output voltage is 8 V. For the same OPAMP, when  $v_1 = v_2 = 1\text{ mV}$ , output voltage is 12 mV. Calculate the CMRR of the OPAMP

Ans: 56.48 dB



# OPAMP equivalent circuit

Practical OPAMP

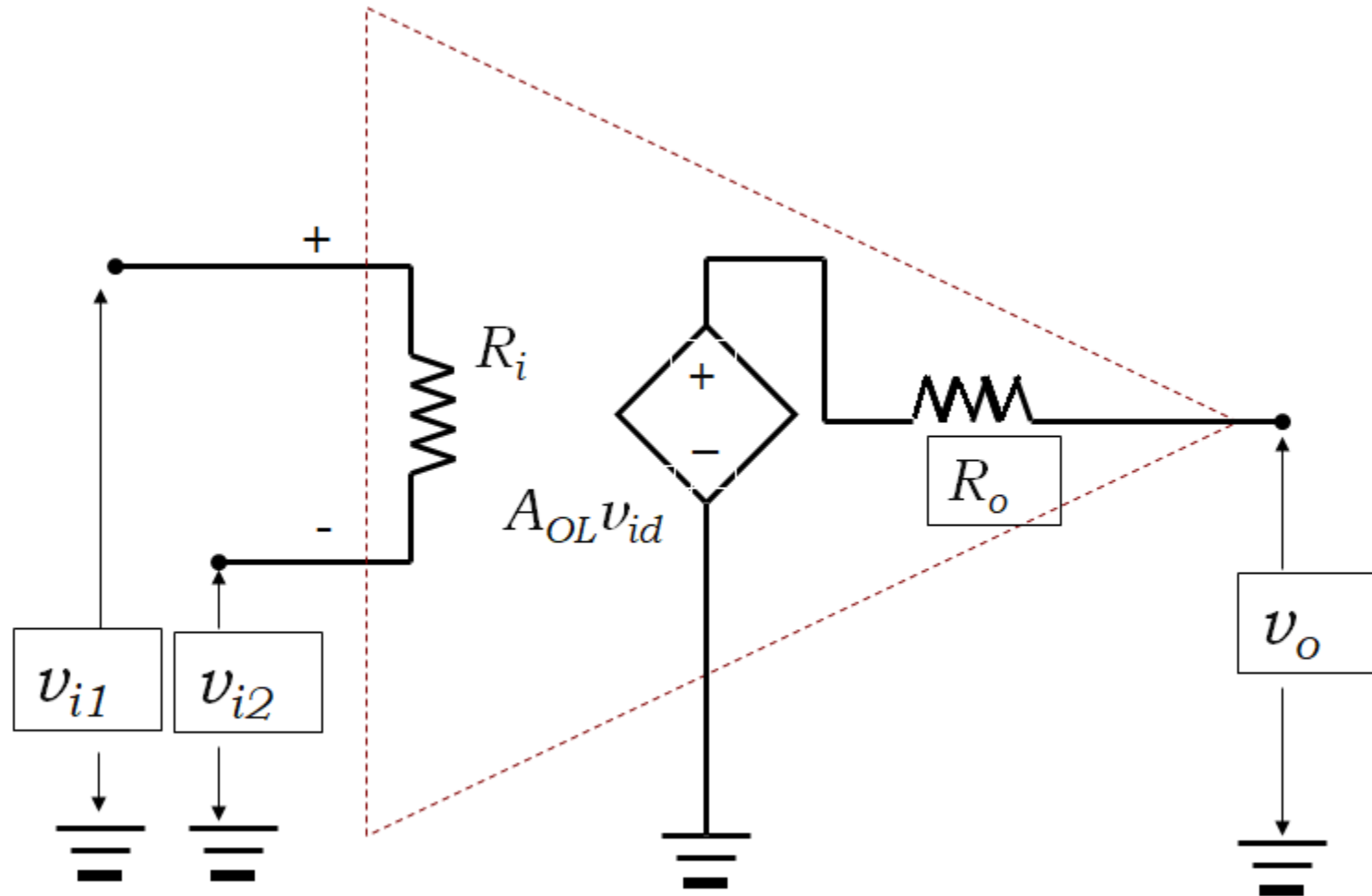

# OPAMP CHARACTERISTICS

- Differential mode gain  $A_d$ 
  - It is the factor by which the difference between the two input signals is amplified by the OPAMP
- Common mode gain  $A_{cm}$ 
  - It is the factor by which the common mode input voltage is amplified by the OPAMP
- Common mode rejection ratio  $CMRR$ 
  - Is the ratio of  $A_d$  to  $A_{cm}$  expressed in decibels

## OPAMP CHARACTERISTICS

- Input resistance  $R_i$ 
  - It is the equivalent resistance measured between the two input terminals of OPAMP
- Output resistance  $R_o$ 
  - It is equivalent resistance measured between output terminal and ground
- Bandwidth
  - It is the range of frequency over which the gain of OPAMP is almost constant

# OPAMP CHARACTERISTICS

- Output offset voltage  $V_{oo}$ 
  - It is the output voltage when both input voltages are zero
  - Denoted as  $V_{oo}$
- Input offset voltage  $V_{io}$ 
  - It is the differential input voltage that must be applied at the input terminals in order to make output voltage equal to zero
  - $V_{io} = |v_{dc1} - v_{dc2}|$  for  $v_o = 0$

# OPAMP CHARACTERISTICS

- Input offset current  $I_{io}$ 
  - It is the difference between the currents in the input terminals when both input voltages are zero
  - $I_{io} = | I_1 - I_2 |$  when  $v_1 = v_2 = 0$
- Input bias current  $I_{ib}$ 
  - It is the average of the currents in the input terminals when both input voltages are zero
  - $I_{ib} = (I_1 + I_2) / 2$  when  $v_1 = v_2 = 0$

## OPAMP CHARACTERISTICS

- Slew rate  $SR$ 
  - It is the maximum rate of change of output voltage with respect to time
  - Slew rate has to be very high if OPAMP has to operate efficiently at high frequencies
- Supply voltage rejection ratio  $SVRR$ 
  - It is the maximum rate at which input offset voltage of OPAMP changes with change in supply voltage

# OPAMP CHARACTERISTICS

## ■ Practical characteristics of 741C OPAMP

- Differential mode gain is 200,000
- CMRR is 90 dB
- Input resistance is 2 M $\Omega$
- Output resistance is 75  $\Omega$
- Unity-gain Bandwidth is 1 MHz
- Slew rate is 0.5 V /  $\mu$ s
- Output offset voltage is 1 mV
- Input offset current is 20 nA
- Input bias current is 80 nA

## ■ Ideal OPAMP

- Infinite differential mode gain
- Zero common mode gain
- Infinite CMRR
- Infinite input resistance
- Zero output resistance
- Infinite bandwidth
- Infinite slew rate
- Zero input offset voltage
- Zero input offset current
- Zero output offset voltage


# **OPERATIONAL AMPLIFIER (OP-AMP)**



## CLOSED-LOOP CONFIGURATIONS

- Open-loop voltage gain of OPAMP is very high; such high gain is not required in most applications
- In order to reduce gain, a part of output signal is fed back to the inverting input terminal (called negative feedback)
- Many other OPAMP characteristics are improvised with this


# INVERTING AMPLIFIER

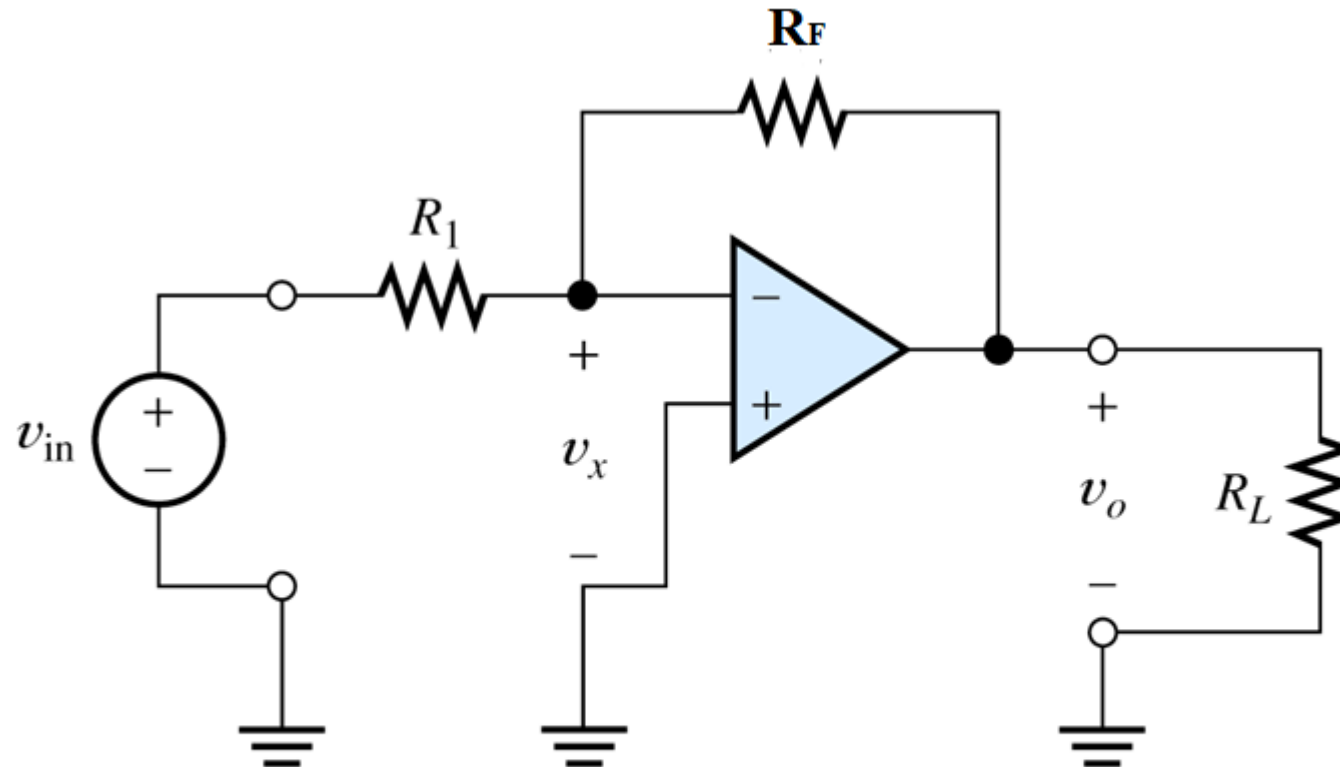

## INVERTING AMPLIFIER

- Input is applied to inverting terminal
- Non-inverting is grounded
- Feedback is given to inverting terminal through resistor  $R_F$
- Assuming  $v_o$  is less than  $V_{CC}$   
since  $A_d$  is very high,  $v_{id}$  should be very small;  $v_{id}$  taken as almost zero
- Current entering OPAMP input terminal is almost zero

# INVERTING AMPLIFIER

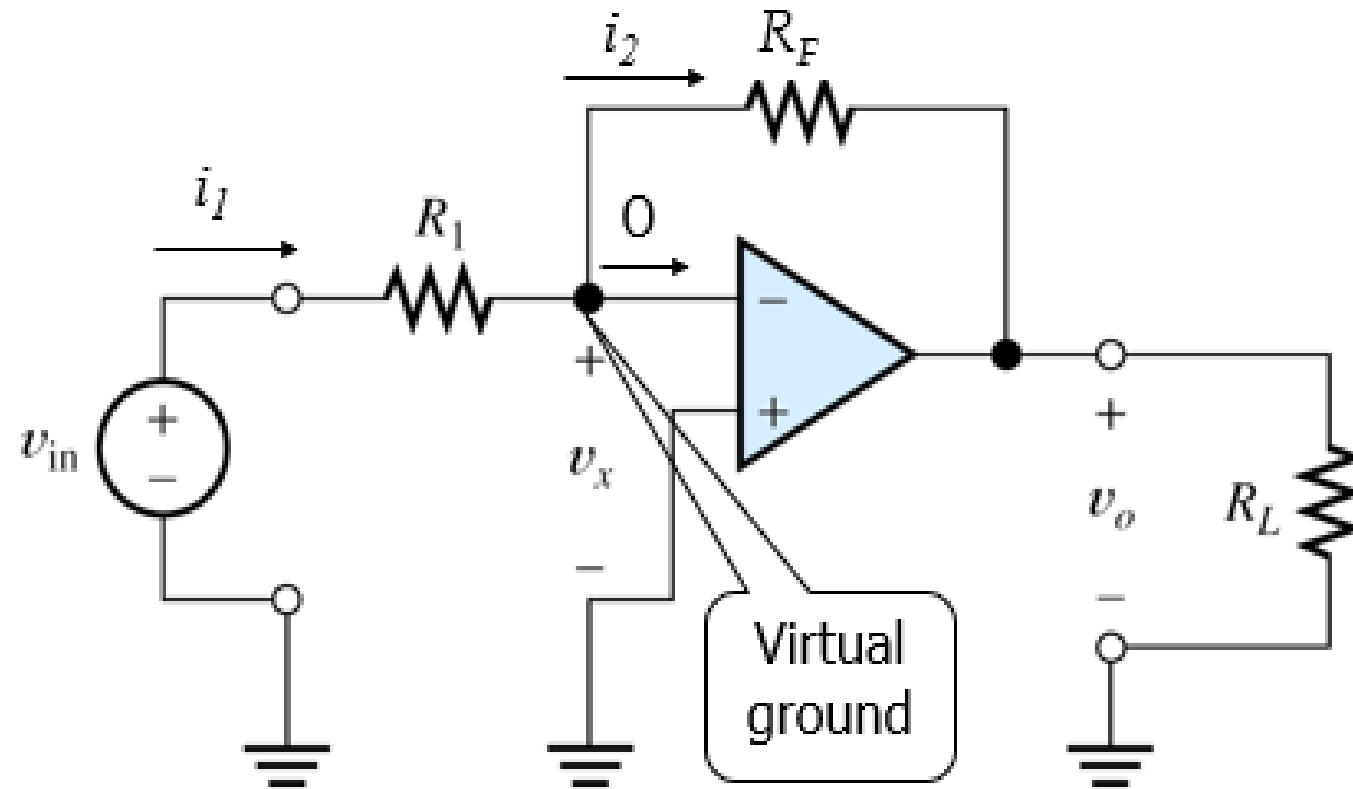

# INVERTING AMPLIFIER

$$i_1 = \frac{v_{in} - 0}{R_1} = \frac{v_{in}}{R_1}$$


$$i_2 = \frac{0 - v_o}{R_F} = \frac{-v_o}{R_F}$$

$$i_1 = i_2$$

$$\frac{v_{in}}{R_1} = \frac{-v_o}{R_F}$$

$$v_o = -v_{in} \frac{R_F}{R_1}$$
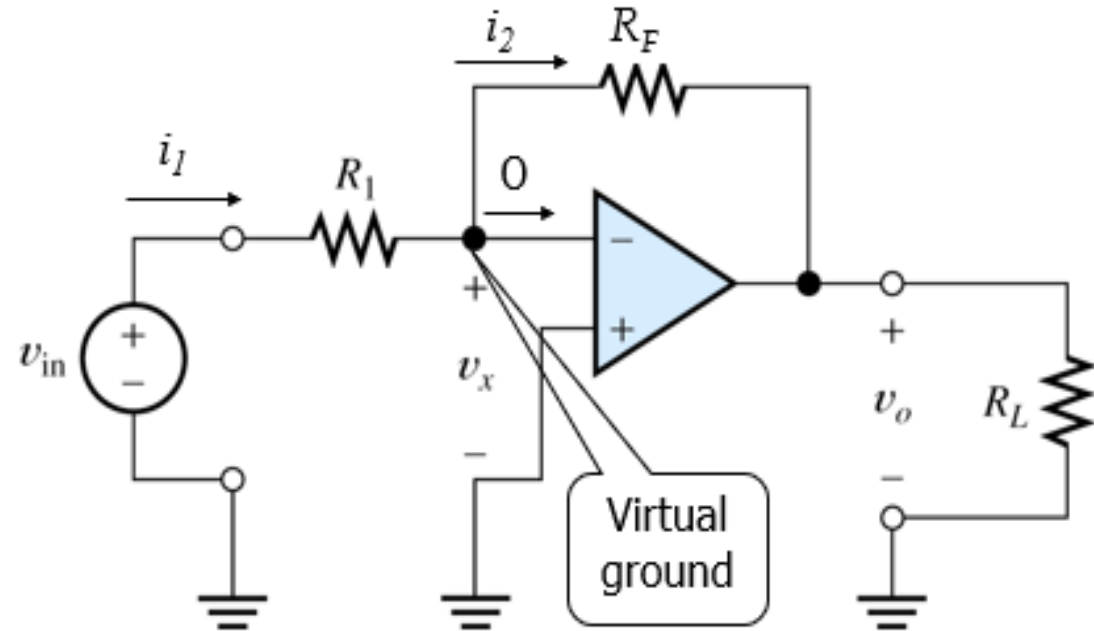
$$A_V = \frac{v_o}{v_{in}} = -\frac{R_F}{R_1}$$




## PROBLEMS


1. For an inverting amplifier using OPAMP,  $R_1=1\text{K}$ ,  $R_F=100\text{K}$ ,  $v_{in}=0.1\sin(\omega t)$ . Find  $v_o$ .
2. For an inverting amplifier,  $R_1=10\text{K}$ ,  $R_F=100\text{K}$ . Calculate  $v_o$  if  $v_i = 25\text{ mV dc}$ .
3. An ac signal of rms value  $2\text{ mV}$  needs to be amplified to  $1.024\text{ V rms}$ ,  $180$  degree phase shifted. Design a suitable amplifier choosing  $R_1=1.2\text{K}$
4. Design an amplifier to get an output amplified by 25 times of the input signal .
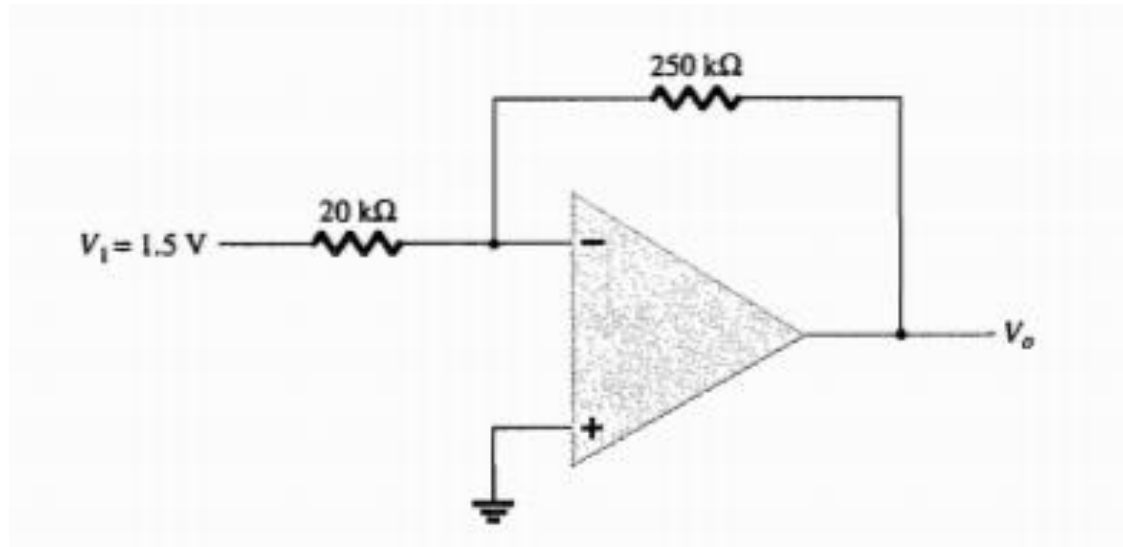
## EXAMPLE 5

Find the output voltage  $V_o$  for the following circuit, where  $V_{in}$  is the input voltage .




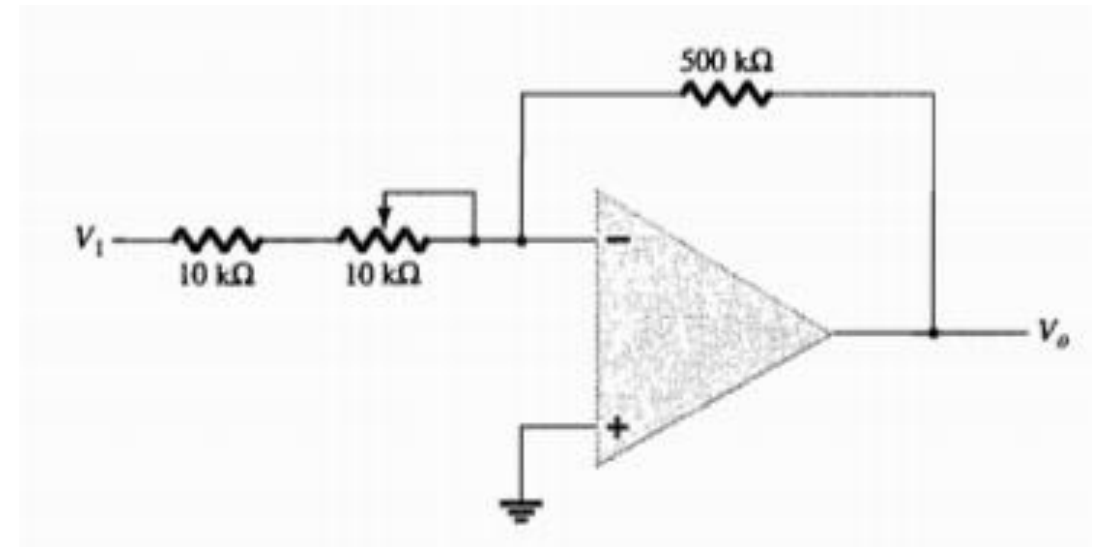Find the range of output voltage gain adjustment for the following circuit, where  $V_i$  is the input voltage .



## EXAMPLE 6

What input voltage will result if an output voltage  $V_o = 2V$  for the following circuit, where  $V_i$  is the input voltage .

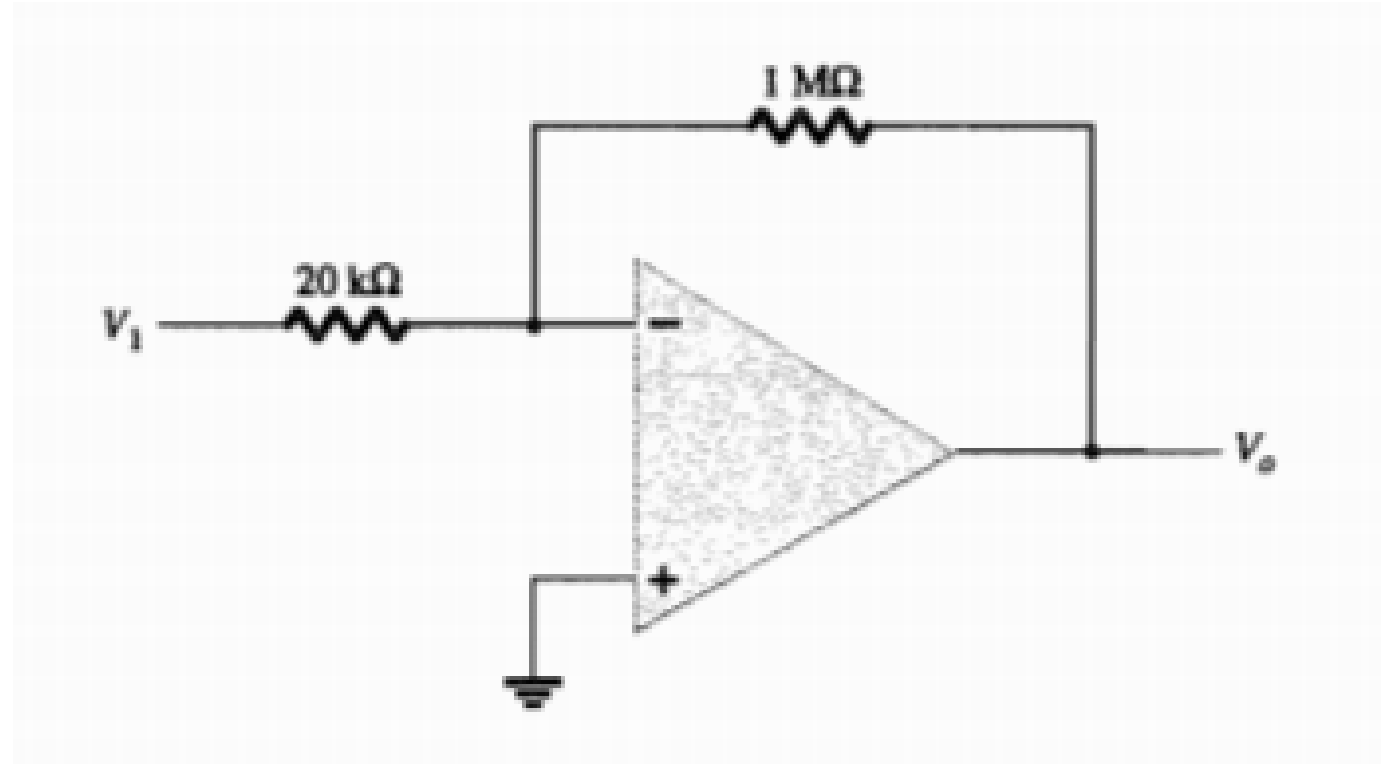



**EXAMPLE 7:** Calculate the output voltage  $V_o$  for the following circuit, where  $V_i$  is the input voltage


Solution :

The output of Op-Amp A1 is  
(say)

$$v_{o1} = -\frac{100}{20} v_i = -5v_i$$


The output of Op-Amp A2 is
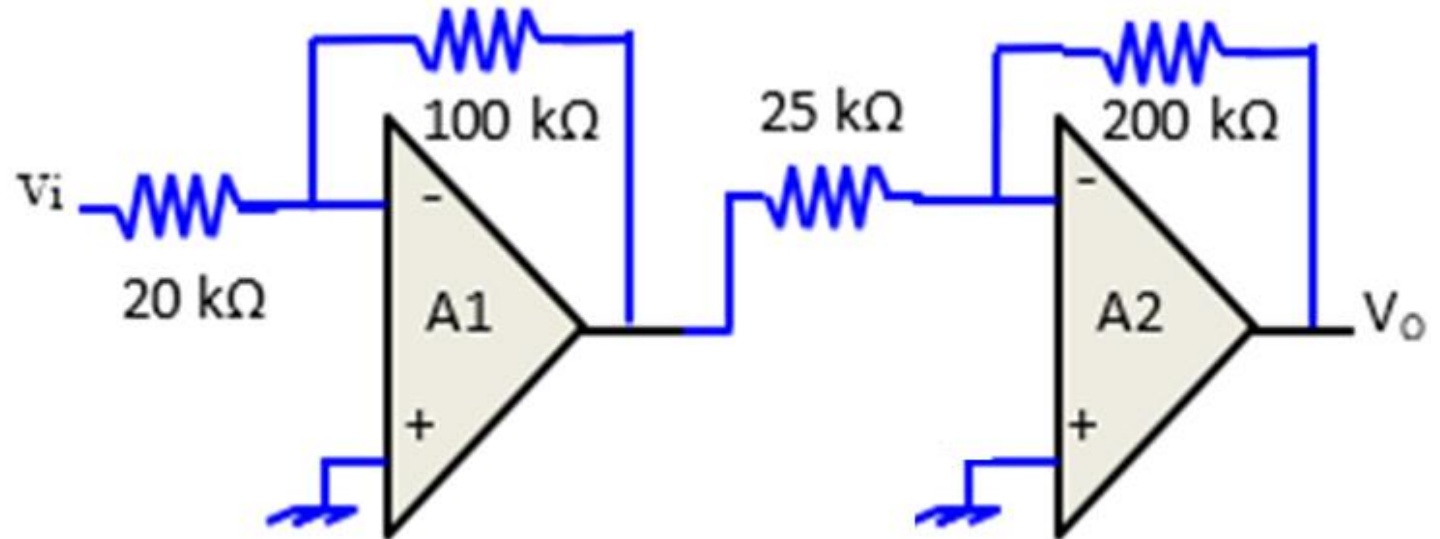
$$\begin{aligned} &= -\frac{200}{25} v_{o1} \\ &= -8(-5v_i) \\ &= 40v_i \end{aligned}$$


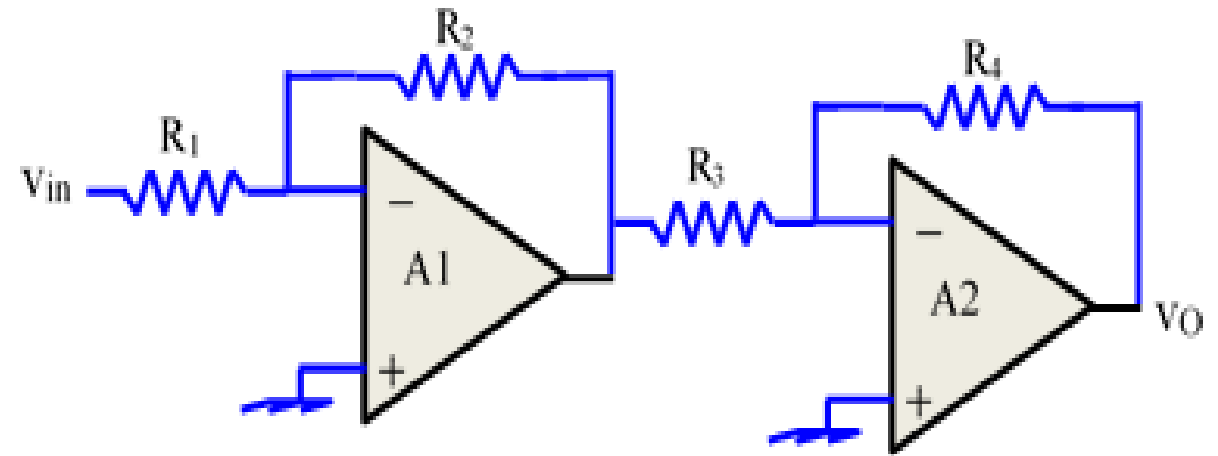
## EXAMPLE 8


Find an expression for the output voltage  $V_o$  for the following circuit, where  $V_{in}$  is the input voltage .



## EXAMPLE 9

Find the expression for output voltage  $V_o$  of the following circuit.

Soln.  
Apply KCL.

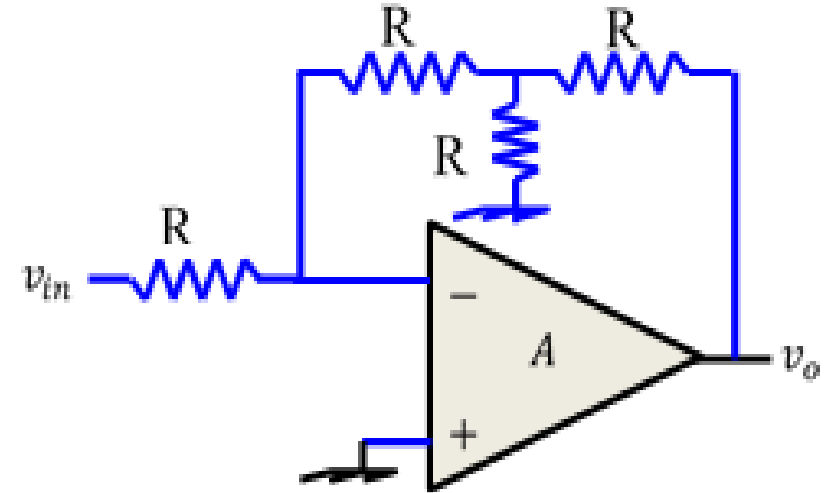




Thank you

# **OPERATIONAL AMPLIFIER (OP-AMP)**


# NON-INVERTING AMPLIFIER

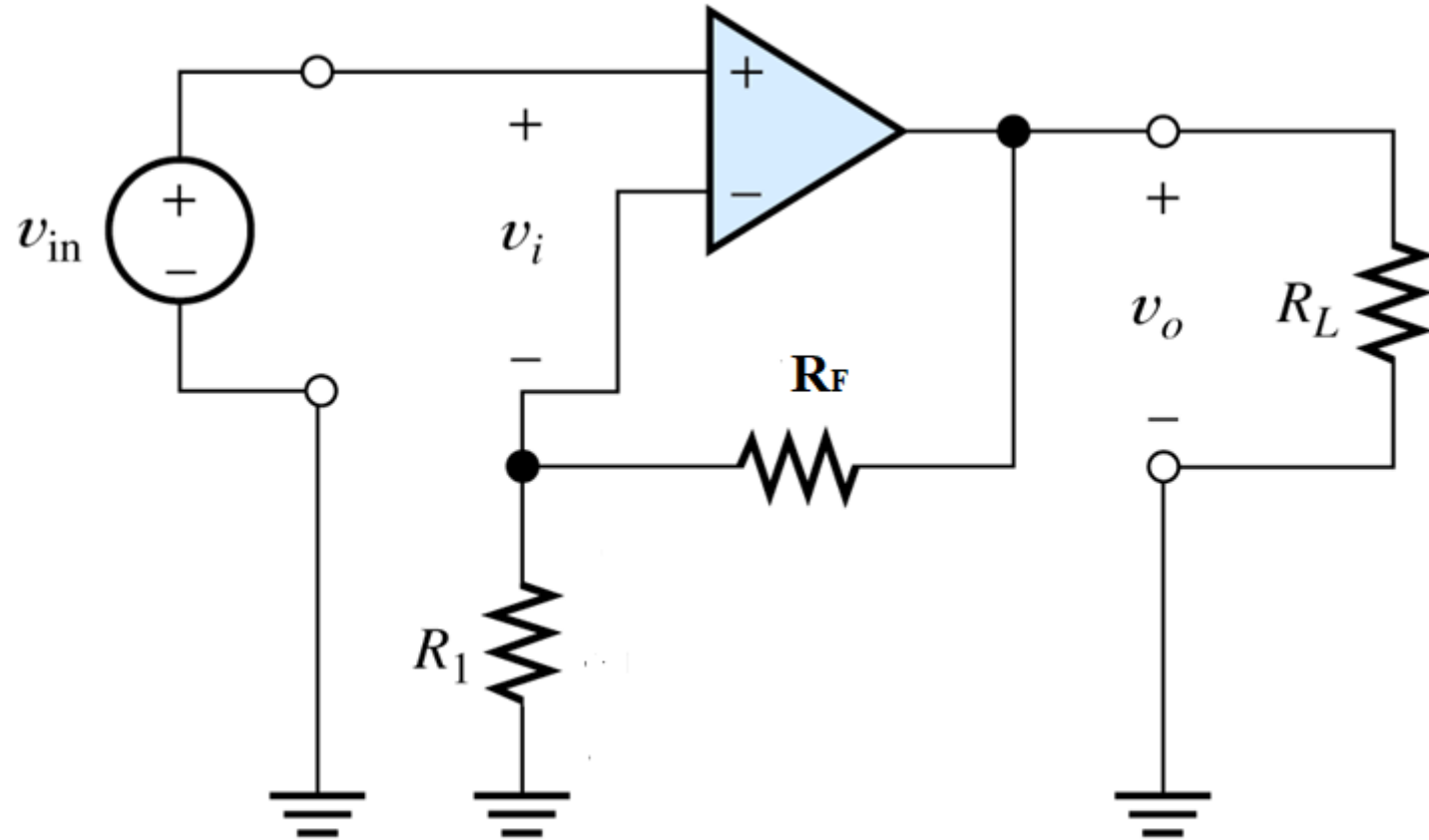

# NON-INVERTING AMPLIFIER

- Input is applied to non-inverting terminal
- Feedback is given to inverting terminal
- Output voltage will be in-phase with input voltage
- Here again, the following assumptions are made
  - Since  $A_d$  is very high,  $v_{id}$  should be very small;  $v_{id}$  taken as almost zero
  - Current entering OPAMP input terminal is almost zero

# NON-INVERTING AMPLIFIER

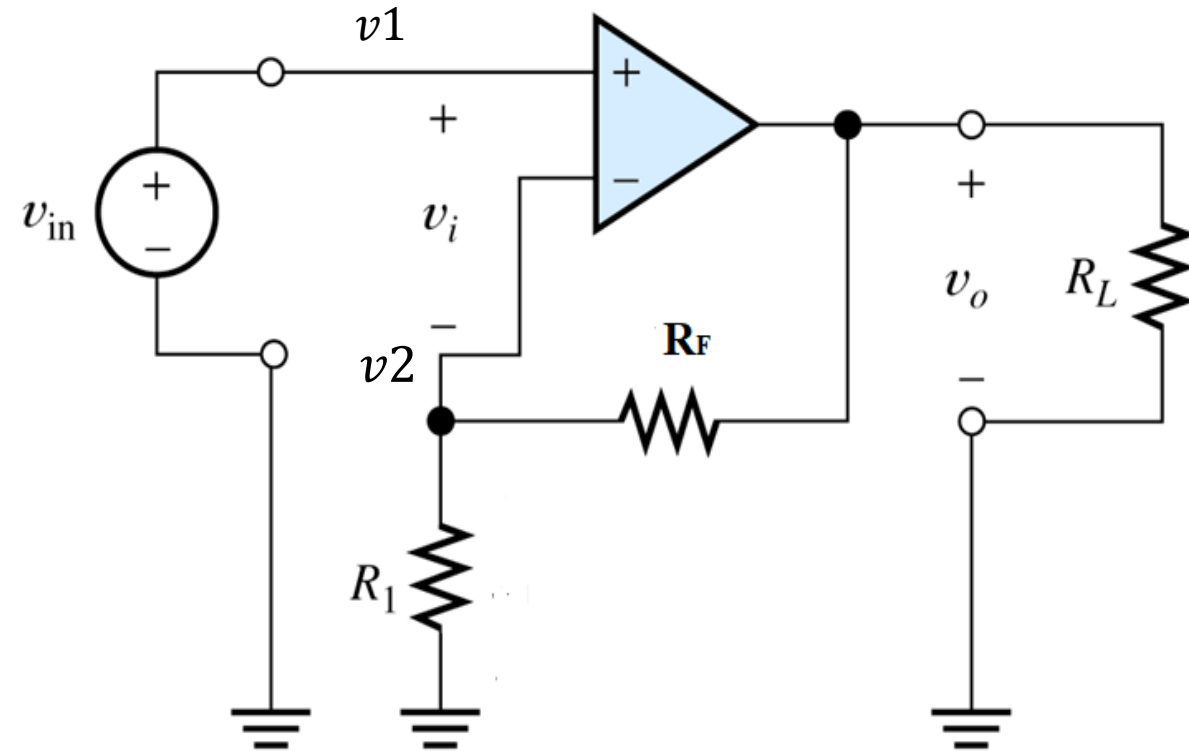



# NON-INVERTING AMPLIFIER

$$v_{id} = 0$$

$$v_1 = v_2 = v_{in}$$


$$i_1 = \frac{v_2}{R_1} = \frac{v_{in}}{R_1}$$

$$i_2 = \frac{v_o - v_2}{R_F} = \frac{v_o - v_{in}}{R_F}$$

$$i_1 = i_2$$

$$\frac{v_{in}}{R_1} = \frac{v_o - v_{in}}{R_F}$$
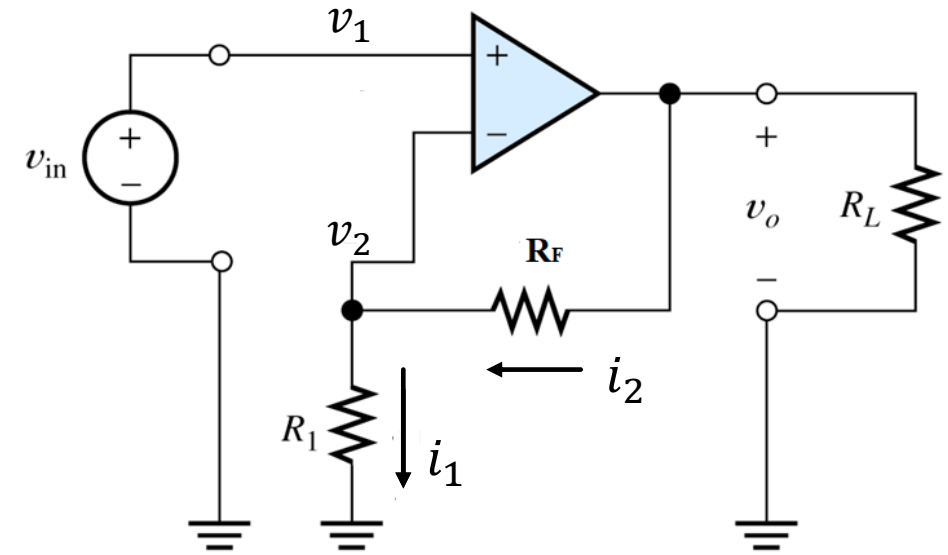
$$v_o = v_{in} \left( 1 + \frac{R_F}{R_1} \right)$$




## PROBLEMS

1. For an non-inverting amplifier using OPAMP,  $R_1=1K$ ,  $R_F=100K$ ,  $v_{in}=0.1\sin(\omega t)$ . Find  $v_o$ .
2. For a non-inverting amplifier,  $R_1=10K$ ,  $R_F=100K$ . Calculate  $v_o$  if  $v_i = 25$  mV dc.
3. An ac signal of rms value 2 mV needs to be amplified to 1.2 V rms, and output must be in same phase as input. Design a suitable amplifier choosing  $R_1=2K$

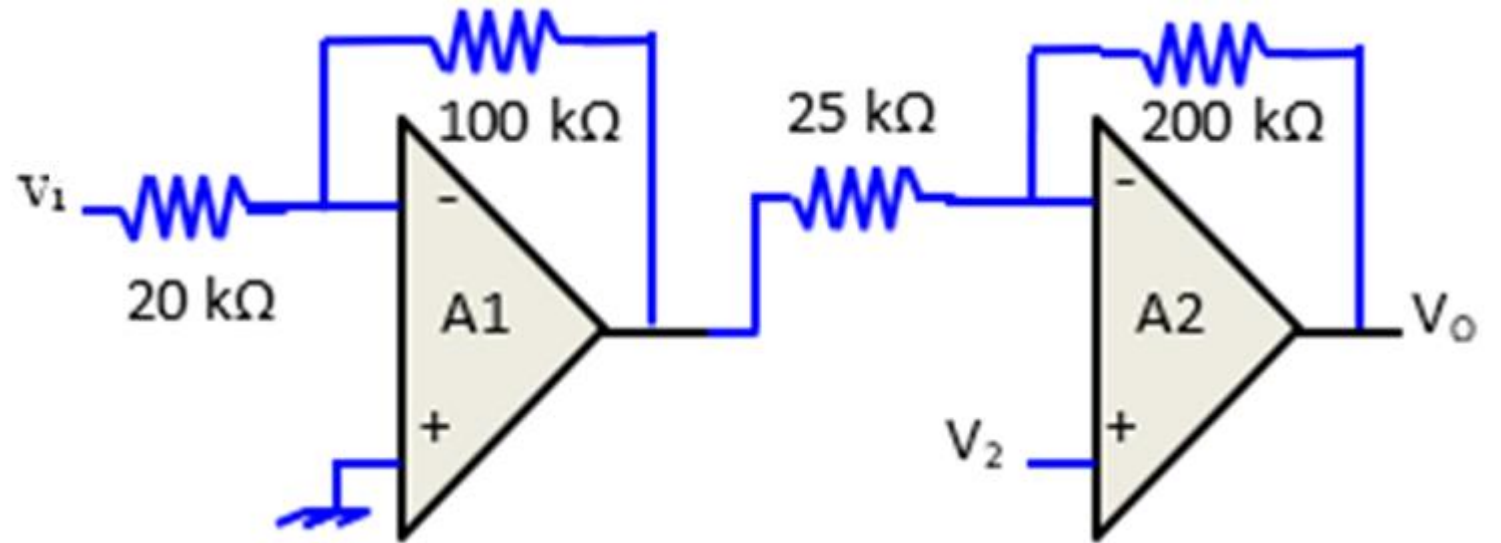
## EXAMPLE 4

Find the output voltage  $V_O$  for the following circuit if  $v_1 = 2\text{V} = V_2$ .



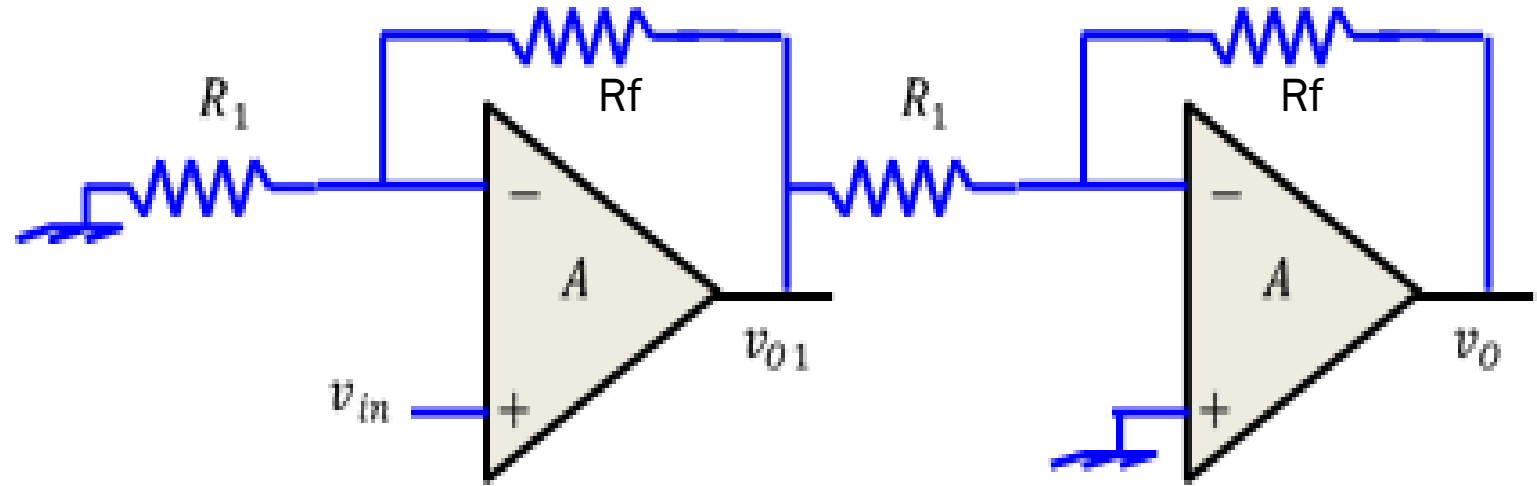
## EXAMPLE 5

Find the output voltage  $V_O$  for the following circuit if  $V_{in} = 2V$ ,  $R_1 = 2k$  and  $R_f = 10k$ .



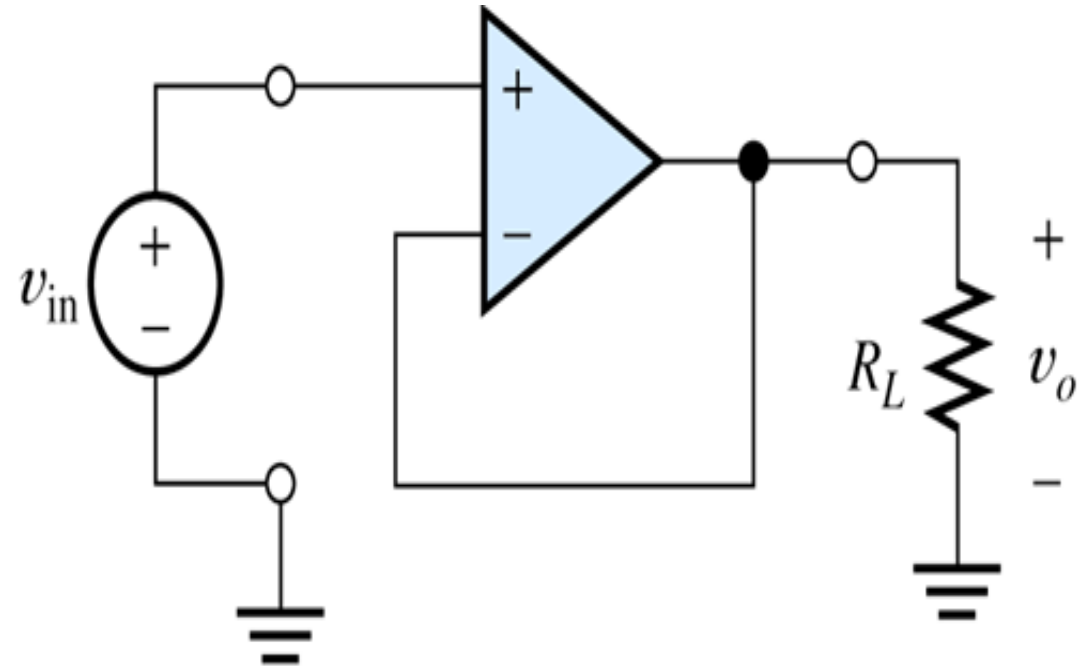
## VOLTAGE FOLLOWER

- Special case of non-inverting amplifier where  $R_F=0$
- Voltage gain is unity.  $v_o = v_{in}$
- Has very high input resistance and very low output resistance; Used as buffer for impedance matching



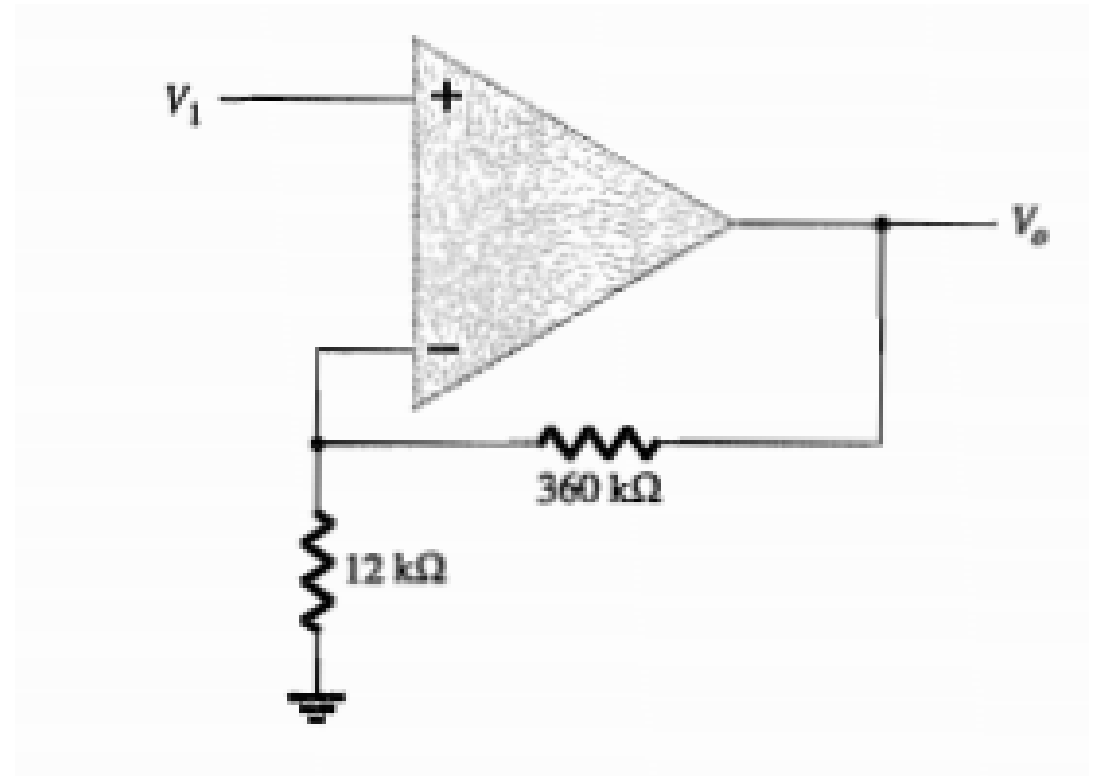
## EXAMPLE 6

Find the output voltage  $V_0$  for the following circuit if  $v_1 = 2\text{V} = V_2$ .



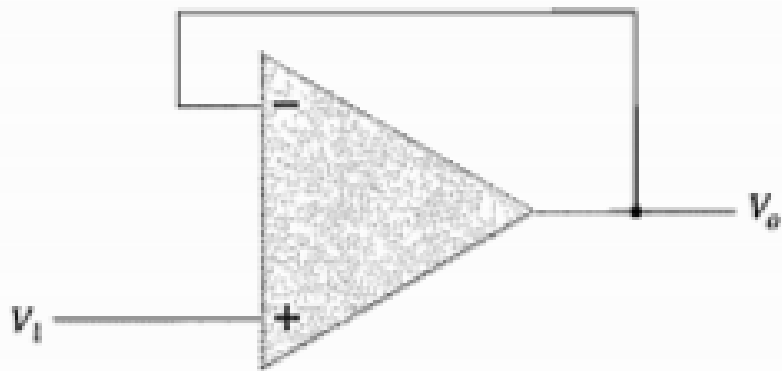
## EXAMPLE 7

Find the output voltage  $V_o$  for the following circuit if  $v_1 = 2\text{ V}$ .




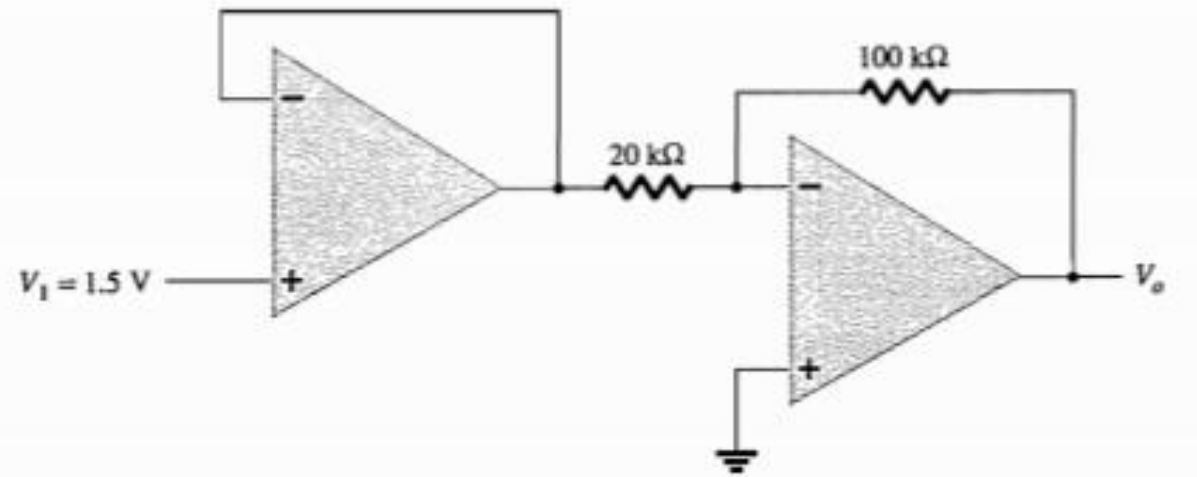Find the output voltage  $V_o$  for the following circuit.


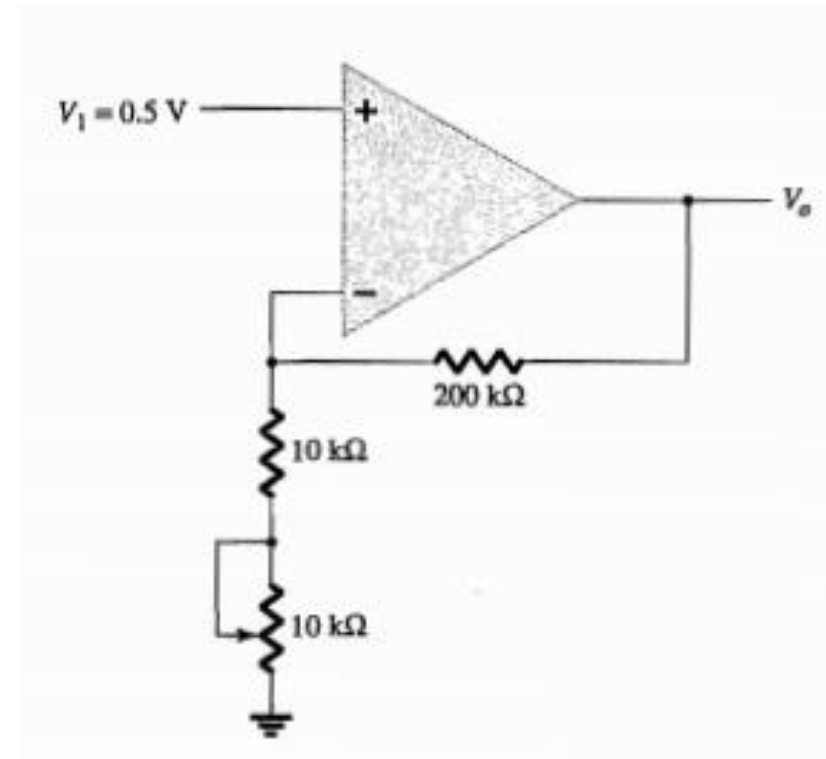
## EXAMPLE 8

Calculate the range of output voltage for the circuit.





■ Thank You